

Praxissemesterbericht  
**"Inbetriebnahme eines Spartan 3E FPGA  
Evaluations Boards"**

Torsten Krause

10. Oktober 2008



## Inhaltsverzeichnis

<b>1</b>	<b>Einleitung</b>	<b>4</b>
1.1	Die Max-Planck-Gesellschaft . . . . .	4
1.2	Das Max-Planck-Institut für Radioastronomie . . . . .	4
1.3	Das Radioteleskop Effelsberg . . . . .	5
<b>2</b>	<b>Grundlagen</b>	<b>6</b>
2.1	Field Programmable Gate Array . . . . .	6
2.2	Very High Speed Integrated Circuit Hardware Decryption Language . . . . .	6
<b>3</b>	<b>Aufgabenstellung</b>	<b>7</b>
3.1	Takt teilen . . . . .	8
3.2	Ampelschaltung . . . . .	9
3.3	Binär zählen . . . . .	10
3.4	Drehinkrementgeber . . . . .	11
3.5	Schnittstelle EIA 232 . . . . .	13
3.5.1	Konstante senden . . . . .	13
3.5.2	Variable senden . . . . .	15
3.5.3	Senden mehrerer Zeichen . . . . .	16
3.5.4	Konstante empfangen . . . . .	17
3.5.5	Senden und Empfangen . . . . .	18
3.6	LC-Display . . . . .	19
3.7	Vorverstärker . . . . .	20
3.7.1	Verstärkung einstellen . . . . .	20
3.7.2	Verstärkung anzeigen . . . . .	22
<b>4</b>	<b>Zusammenfassung</b>	<b>23</b>
<b>A</b>	<b>Anhang</b>	<b>24</b>
A.1	Takt teilen . . . . .	24
A.2	Ampelschaltung . . . . .	26
A.3	Binär zählen . . . . .	34
A.4	Drehinkrementgeber . . . . .	39
A.5	Konstante senden . . . . .	45
A.6	Variable senden . . . . .	49
A.7	Senden mehrerer Zeichen . . . . .	57
A.8	Konstante empfangen . . . . .	66
A.9	Senden und Empfangen . . . . .	70
A.10	LC - Display . . . . .	83
A.11	Verstärkung einstellen . . . . .	90
A.12	Verstärkung anzeigen . . . . .	97



## Abbildungsverzeichnis

1	Radioteleskop Effelsberg . . . . .	5
2	FPGA . . . . .	6
3	Xilinx Spartan 3E . . . . .	7
4	Signalverlaufplan: Takt teilen . . . . .	9
5	Signalverlaufplan: Ampelschaltung . . . . .	10
6	Signalverlaufplan: Binär zählen . . . . .	11
7	Funktionsdiagramm Rotary-Contact-Filter . . . . .	12
8	Signalverlaufplan: Drehinkrementgeber . . . . .	12
9	EIA-232 Übertragung . . . . .	14
10	Signalverlaufplan: Konstante senden . . . . .	14
11	Signalverlaufplan: Variable senden . . . . .	15
12	Signalverlaufplan: Senden mehrerer Zeichen . . . . .	16
13	Signalverlaufplan: Konstante empfangen . . . . .	17
14	Signalverlaufplan: Senden und Empfangen . . . . .	18
15	Initialisierung . . . . .	19
16	ASCII-Tabelle . . . . .	19
17	Signalverlaufplan: LC-Display . . . . .	20
18	Timing-Diagramm SPI . . . . .	21
19	Signalverlaufplan: Verstärkung einstellen . . . . .	21
20	LC-Display . . . . .	22
21	Signalverlaufplan: Verstärkung anzeigen . . . . .	22



## 1 Einleitung

### 1.1 Die Max-Planck-Gesellschaft

Die Max-Planck-Gesellschaft zur Förderung der Wissenschaften e. V. (kurz MPG) wurde am 26. Februar 1948 gegründet. Sie ist eine unabhängige und gemeinnützige Forschungsorganisation.

Gefördert werden vorrangig die 81 eigenständigen Forschungsinstitute, so z.B. für Plasmaphysik, für experimentelle Medizin oder für terrestrische Mikrobiologie.

Diese forschen in „Natur-, Bio-, Geistes- und Sozialwissenschaften im Dienste der Allgemeinheit“.

Einige Max-Planck-Institute stellen ihre aufwendigen Einrichtungen und Geräte zur Mitnutzung den Forschern deutscher Universitäten zur Verfügung.

Insgesamt haben die 81 Institute rund 12.600 Mitarbeiter und 11.300 Doktoranten, Postdoktoranten, Gastwissenschaftler und studentische Hilfskräfte.

### 1.2 Das Max-Planck-Institut für Radioastronomie

Die Arbeit des 1966 gegründeten Max-Planck-Instituts für Radioastronomie (kurz: MPIfR) beruht wesentlich auf Beobachtungen, die am Radio-Observatorium Effelsberg durchgeführt werden.

Da die vom Radioteleskop empfangenen Signale sehr schwach sind und das Umgebungsrauschen um ein vielfaches stärker ist, entwickelt die Elektronikabteilung extrem rauscharme, stark gekühlte Verstärker.

Regelmässig beteiligt sich das Institut an verschiedenen internationalen Netzwerken, bei denen mit Hilfe vieler Teleskope ein virtuelles Radioteleskop mit einem Durchmesser bis zu mehrerer Tausend Kilometern simuliert wird.

Diese Radiointerferometriebeobachtungen erreichen die höchsten räumlichen Auflösungen die zur Zeit möglich sind.



### 1.3 Das Radioteleskop Effelsberg

Das 100m-Radioteleskop Effelsberg (Abb.1) ist das zweitgrößte vollbewegliche Teleskop der Welt. Es ist seit 1972 in Betrieb und wird seitdem für radioastronomische Beobachtungen genutzt.

2352 Paneelen bilden die  $7850m^2$  große Antennenoberfläche. Das Teleskop hat ein Gesamtgewicht von 3200t und kann mit einer Genauigkeit von 0,3 mm in 12 Minuten eine  $360^\circ$  Drehung vollziehen.

Radiowellen mit Wellenlängen zwischen 90 cm und 3,5 mm können empfangen und ausgewertet werden. Der Standort wurde in einem Tal mit geringer Bevölkerung gewählt um den Einfluss von Fremdstrahlung zu minimieren.

Hauptbeobachtungsziele sind:

- Pulsare
- Schwarze Löcher
- Galaxiekern
- kalte Gas- und Staubwolken



Abbildung 1: Radioteleskop Effelsberg



## 2 Grundlagen

### 2.1 Field Programmable Gate Array

Ein Field Programmable Gate Array (kurz: FPGA) ist ein Baustein, mit dessen Hilfe logische Schaltungen verwirklicht werden. Ein FPGA besteht hauptsächlich aus drei Komponenten:

- matrixförmig angeordnete Logikblöcke
- einem Verbindungsnetz (Routing-Kanäle)
- Ein- und Ausgangsblöcke

Die programmierte Funktion wird aus den Logikblöcken, meist Flip-Flops und Lookup-Tables, über die Routing-Kanäle verknüpft. Wobei die Flip-Flops als Speicher dienen, um den aktuellen Signalwert im nächsten Takt weiterverarbeiten zu können und die Lookup-Tables die Funktion mit Hilfe der Grundlogikfunktionen (AND, OR, XOR, ...) „berechnet“. Abbildung 2 zeigt das FPGA auf dem Spartan 3E.

 


Abbildung 2: FPGA

### 2.2 Very High Speed Integrated Circuit Hardware Description Language

Durch die Hardwarebeschreibungssprache „Very High Speed Integrated Circuit Hardware Description Language“ (kurz: VHDL) ist es möglich, digitale Systeme zu beschreiben. Selbst komplizierte Schaltungen können übersichtlich dargestellt und simuliert werden.

Entwickelt wurde VHDL um eine standardisierte Dokumentation von Funktion und Struktur integrierter Schaltung zu erhalten. So ist es möglich bestehende Programme in verschiedene Bausteine zu laden oder mit verschiedenen Programmen zu simulieren.



### 3 Aufgabenstellung

#### „ Inbetriebnahme eines Spartan 3E FPGA Evaluations Boards “

Aufgabe des Praxissemesters war die Datenerfassung und Verarbeitung mit einem FPGA. Dazu wurde mir das Starterkit Spartan 3E der Firma Xilinx (Abb.3) zur Verfügung gestellt.

 


Abbildung 3: Xilinx Spartan 3E

#### **Anmerkung:**

Um die Grundlagen der FPGA-Programmierung in VHDL zu erarbeiten, wurde nicht ein großes Projekt, sondern viele Kleine verwirklicht. Am Ende jedes Projekts wurde ein Signalverlaufplan erstellt. Ein Signalverlaufplan verdeutlicht den Aufbau des Programms und den Verlauf der einzelnen Signale. Hierbei steht das große grüne Rechteck für das Projekt. Jedes weiße Rechteck symbolisiert eine Instanz, welche durch Signalpfade verbunden sind. Die Signalnamen sind in Pink, die Ein- und Ausgänge der Instanzen in Grün und die Ein- und Ausgänge des Projekts in Blau beschrieben.



### 3.1 Takt teilen

#### Aufgabenstellung:

Runterteilen des vom FPGA-Board gelieferten Taktsignals um einen beliebigen Faktor

#### Beschreibung:

Das FPGA-Board ist mit 50 MHz getaktet. Dieser Takt wird um den Faktor 25.000.000 geteilt und auf ein LED gelegt, sodass diese im Takt blinkt.

Wie im Signalverlaufplan dargestellt, besteht das Projekt lediglich aus einer Instanz und je einem Ein- bzw. Ausgangssignal. Das Eingangssignal ist das ungeteilte und das Ausgangssignal das geteilte Clock-Signal.

In den Zeilen 5 bis 8 der Instanz „TOP“ wurden die Bibliotheken eingebunden. Die hier verwendeten sind Standard und wurden nicht verändert.

Es folgt (Zeilen 10 bis 13) die Entity, diese beschreibt die Schnittstellen nach Außen. In der Entity sind Signale deklariert, denen jeweils eine Richtung zugeordnet wird. Es gibt drei gebräuchliche Richtungen: in (Eingangssignal), out (Ausgangssignal) und inout (Bidirektionales Signal).

Das Signal „clock“ ist STD\_LOGIC, d.h. es nimmt nur die binären Werte 1 oder 0 an. In diesem Signaltyp sind auch noch andere Signalwerte definiert, wie z.B. H (High), L (Low) oder Z (Hochohmig). In allen folgenden Projekten werden nur die Signalwerte 1 und 0 genutzt.

Das Signal „leds\_out“ ist vom Typ STD\_LOGIC\_VECTOR, also ein binärer Bus der Breite 8. Dieser Bus hätte anstatt wie hier abfallend (7 downto 0) auch aufsteigend (0 to 7) bezeichnet werden können. Hierbei wird nur die Durchnummerierung der einzelnen Bits des Vektors festgelegt.

Das restliche Programm (Zeilen 15 bis 29) ist die Architektur, welche das Innenleben, d.h. die Funktionalität des VHDL-Codes, beschreibt. Jeder Entity muss mindestens eine Architecture zugeordnet sein.

In dieser Architecture ist ein Prozess verwirklicht. In einem Prozess werden aus den Eingangssignalen die Ausgangssignale mit Hilfe der Signalzuweisungen errechnet. In Zeile 17 steht die „Sensitivity-Liste“, bei jeder Änderung eines der hier genannten Signale wird der Prozess einmal durchlaufen.

Im User-Constraint-File (kurz UCF) werden, die in der Entity beschriebenen Signale mit den physikalischen Ein- und Ausgangspins des FPGAs verbunden.



 


Abbildung 4: Signalverlaufplan: Takt teilen

## 3.2 Ampelschaltung

### Aufgabenstellung:

Realisierung einer Ampelschaltung, einbinden mehrerer Instanzen

### Beschreibung:

Das Programm realisiert eine einfache Ampelschaltung mit einer Reset-Funktion. Das Projekt besteht aus der Top-Entity und drei Instanzen. In der Top-Entity werden die Signalkopplungen von mehreren Komponenten in einer Architektur erzeugt, also nur die Schnittstellen der einzelnen Instanzen untereinander und zu den Systemgrenzen. In diesem Projekt sind zwei Top-Entities vorhanden, „Schem“ und „Top“, die von der Funktionalität identisch sind. „Schem“ wurde mit Hilfe einer Funktion von ISE aus einer erstellten Grafik erzeugt. ISE ist die von Xilinx mitgelieferte Entwicklungsumgebung. In Zeile 23 der Instanz „Top“ ist ein Signal deklariert, welches nur innerhalb dieser Architektur existiert und nicht mit einem Ein- oder Ausgangspin belegt werden kann.

Die Instanz „Divider“ hat dieselbe Funktion wie die Instanz „Top“ des vorhergehenden Projekts „Takt teilen“.

Das Zählen der positiven Flanken des „runtergeteilten“ Taktes, sowie das zurücksetzen bei einer positiven Signalflanke des Reset-Signals wurde in der Instanz „Counter“ beschrieben.

Die Instanz „stat\_mac“ wurde ebenfalls aus der oben genannten Grafik durch das ISE erzeugt. Diese Funktion ist aber umständlich und bei komplexeren Projekten sehr kompliziert, außerdem ist eine eventuelle Fehlersuche problematisch. Aus diesen Gründen wurde diese Funktion von ISE in den folgenden Projekten nicht mehr genutzt.

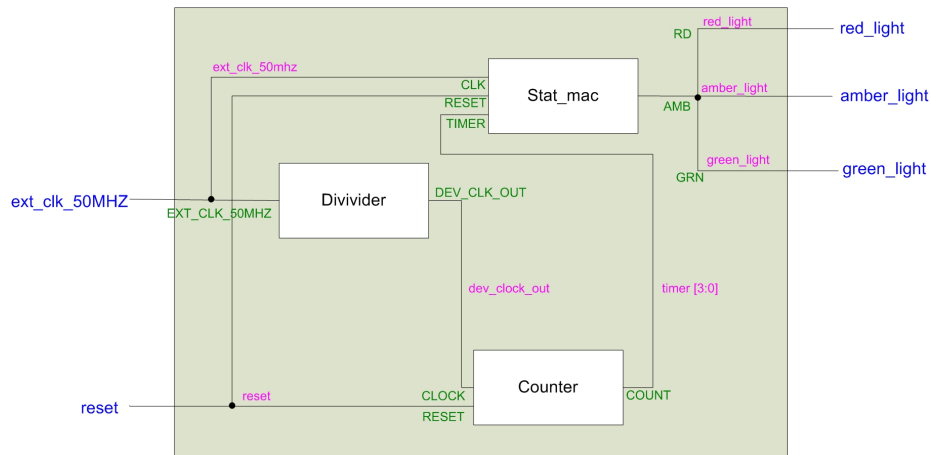


Abbildung 5: Signalverlauffpan: Ampelschaltung

### 3.3 Binär zählen

#### Aufgabenstellung:

Erzeugung eines Ausgangsvektors, diesen verändern und an LEDs ausgeben

#### Beschreibung:

Dieses Projekt enthält wie die vorhergehenden, die Instanz „Divider“ und die Top-Entity „Top“. In der Instanz „Mac“ werden mehrere Funktionen verarbeitet. Es wird ein drei Bit großer Ausgangsvektor erzeugt.

Durch Betätigen des Button East wird dieser auf 0 gesetzt. Wird South gedrückt wird binär hochgezählt und auf West binär runtergezählt.

Außerdem wurden drei Schalter eingebunden die je einem Bit des Ausgangsvektors zugeordnet wurden. Durch Betätigen des Schalters wird das betreffende Bit negiert. Zu beachten ist, dass wenn ein Taster über mehrere positive Flanken gedrückt bleibt, zählt das Programm bei jeder positiven Flanke.

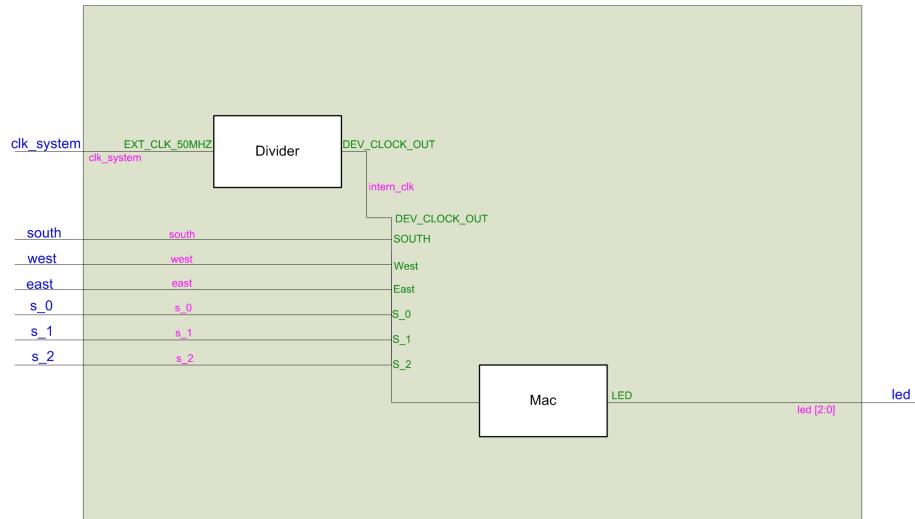


Abbildung 6: Signalverlaufplan: Binär zählen

### 3.4 Drehinkrementgeber

#### Aufgabenstellung:

Drehinkrementgeber implementieren und Prellen unterdrücken

#### Beschreibung:

Die Aufgabe war das Einbinden des Drehinkrementgebers. Das Programm hat, wie im Signalverlaufplan zu erkennen, drei Ausgänge. „Direction“ zeigt an in welche Richtung gedreht wird, „Position“ zeigt binär die Position an und „Test“ legt den geteilten Takt auf eine LED. Der rotary\_contact\_filter wurde eingefügt, da der Drehgeber prellt, d.h. dass die mechanischen Kontakte beim Drehen um eine Position durch Wippbewegungen mehrmals auslösen und so oft eine falsche Richtung anzeigen bzw. mehrere Positionen weiterzählen. Das Prinzip des Filters ist in Abb. 7 dargestellt. Durch geschickten Vergleich von „rotation\_a\_in“ und „rotation\_b\_in“ werden neue Signale erzeugt die zwar nicht den Eingängen gleich sind, aber ein ähnliches Verhalten haben und bei denen dieses Prellen nicht mehr auftritt.

 


Abbildung 7: Funktionsdiagramm Rotary-Contact-Filter

In Zeile 27 der Instanz „Rotary Contact Filter“ ist eine &-Verknüpfung verwendet, dies ist aber nicht die logische AND-Verknüpfung, sondern bildet aus zwei binären Signalen einen Zwei-Bit-Vektor, wobei das erste Bit den Wert des ersten binären Signals hat und das zweite Bit des Vektors den Wert des zweiten Signals annimmt.

Außerdem mussten noch Pullup- und Pulldownwiderstände im User Constraint File ( Zeilen 13 bis 15) aktiviert werden. Der Pullup-Widerstand zieht den Pin auf Betriebsspannung und der Pulldownwiderstand zieht die Spannung auf ground.

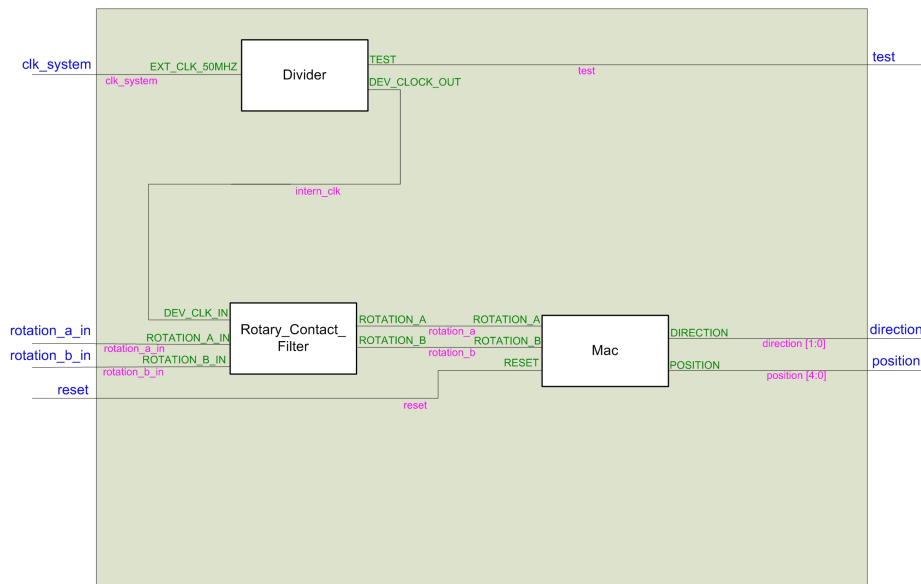


Abbildung 8: Signalverlaufplan: Drehinkrementgeber



## 3.5 Schnittstelle EIA 232

### 3.5.1 Konstante senden

#### Aufgabenstellung:

Senden einer Konstanten und Baudrate festlegen

#### Beschreibung:

Es sollte in diesem Projekt das Senden einer Konstanten über die serielle Schnittstelle EIA-232 programmiert werden. Die Schnittstelle EIA-232 (früher RS-232) ist eine spannungsgesteuerte Schnittstelle, die asynchron und bitseriell arbeitet, d.h. die einzelnen Bits werden nacheinander über eine Leitung gesendet und nach einem Wort kann eine beliebig lange Zeit vergehen, bis das Nächste gesendet wird. Hierbei war zu beachten, dass jedes Datenwort mit einem Startbit (Logisch 0) „angekündigt“ und mit einem Stopbit (Logisch 1) zu versehen war (Abb.9).

Auf das Senden des Paritätsbits, das zur Vermeidung von Fehlern genutzt wird, wurde verzichtet.

Des Weiteren wurde eine negative Logik verwendet. Der Zustand logisch 1 wird in die negative Spannung -15 V und der Zustand logisch 0 in die positive Spannung +15 V übersetzt. Zur Erkennung des Startbits muss immer, wenn nicht gesendet wird, eine logische 1 am Ausgang liegen. Dies wurde im User Constraint File (kurz UCF) in der sechsten Zeile realisiert.

Es war noch die Baudrate zu wählen, diese legt die zeitliche Dauer eines Bits fest. Sender und Empfänger müssen eine gemeinsame Baudrate haben, da sonst keine Kommunikation möglich ist. Die Baudrate wurde auf 9600 Baud festgelegt, was einer Dauer von 104  $\mu$ s entspricht. Im Divider (Zeile 29) musste die richtige Frequenz eingestellt werden.

Diese errechnet sich:

$$f = \frac{t_B \cdot f_{\text{sys}}}{2} = \frac{104\mu\text{s} \cdot 50\text{MHz}}{2} = 2600$$

In der Instanz „Mac“ wurde das Senden umgesetzt. Das Programm sendet nach und nach jedes Bit, der Baudrate entsprechend, an den Ausgang.

In den Zeilen 21 bis 23 der Instanz „Mac“ wurden lokale Signale deklariert. Diese sind nur intern, in dieser Architecture sichtbar und können nicht mit Ein- oder Ausgängen belegt werden. Die beiden Signale „counter\_index“ und „help“ sind vom Typ integer. Integer-Signale nehmen keine binären Werte an, sondern ganzzahlige von -2.147.483.648 bis 2.147.483.647. Dem Signal „help“ wurde in der Instanz „Mac“ Zeile 23 der Anfangswert 0 zugewiesen und sorgt dafür, dass die Bitfolge nur einmal gesendet wird.

Die „elsif“-Anweisung der Instanz „Mac“ (Zeilen 41 bis 52) realisiert zum Einen, dass die Bitfolge nur einmal gesendet wird und zum Anderen, dass die Bitfolge komplett gesendet wird, wenn zwischenzeitlich der Taster losgelassen wurde.

 


Abbildung 9: EIA-232 Übertragung

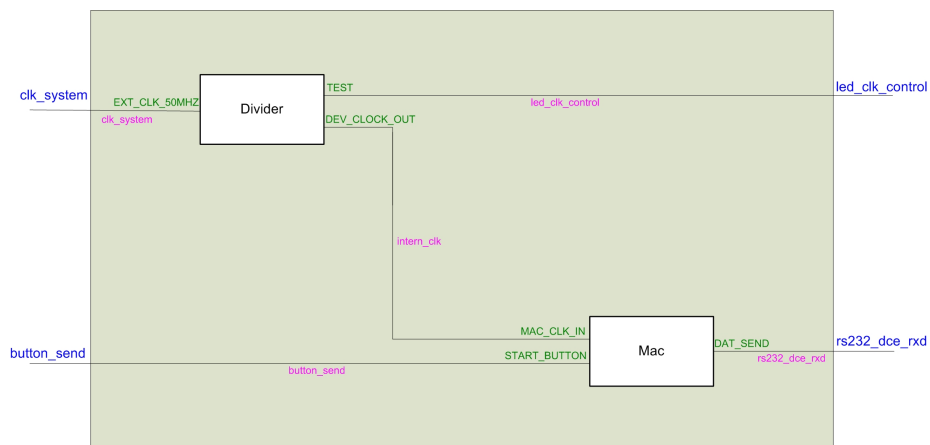


Abbildung 10: Signalverlaufplan: Konstante senden



### 3.5.2 Variable senden

#### Aufgabenstellung:

Senden einer Variablen und Drehinkrementgeber einbinden

#### Beschreibung:

Im nächsten Schritt wurde die Konstante aus dem vorherigen Projekt variabel gestaltet. Zum Einstellen des Signals „dat\_send\_binaer“ wurde der Drehinkrementgeber wieder eingebunden und zur optischen Kontrolle jedes Bit auf eine LED ausgegeben.

In der Instanz „Mac“ Zeile 41 wird das Startbit gesetzt und in den Zeile 32 und 33 das Stopbit.

Die Instanz „Set“ verwirklicht das Auswerten der Drehbewegung und die Verknüpfung des eingestellten Vektors mit den LEDs. Eine Reset-Funktion ist auch implementiert (Zeilen 33 und 34). Das FPGA ermöglicht eine parallele Abarbeitung der einzelnen Instanzen, daher gibt es keine Probleme beim Zusammenführen der Signale.

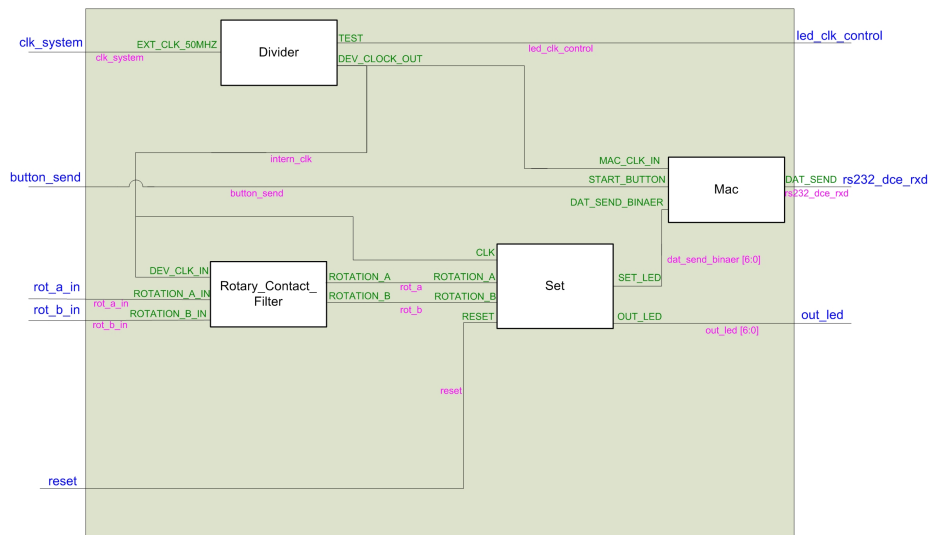


Abbildung 11: Signalverlaufplan: Variable senden



### 3.5.3 Senden mehrerer Zeichen

Aufgabenstellung:

Mehrere Zeichen senden

Beschreibung:

Bei dieser Aufgabe wurde das mehrfach hintereinander senden verschiedener Wörter programmiert.

Hierzu musste das Signal „help“ in der Instanz „Mac“ wieder auf 0 gesetzt werden, sobald der start-button-Knopf gedrückt wird. Dies war aber in der Architecture der Instanz „Mac“ nicht möglich, da es zu Multi-Source-Fehlern kommt, d.h. das ein Signal nicht mehrere Zuweisungen in einer Instanz haben kann.

Deshalb wurde eine weitere Instanz, „set\_help“, implementiert. Diese führt nur diese einfache Zuweisung durch. Das Signal „help“ musste noch von einem lokalen zu einem globalen Signal umdeklariert werden, da es in zwei Instanzen genutzt wurde und dort seinen Wert ändern kann.

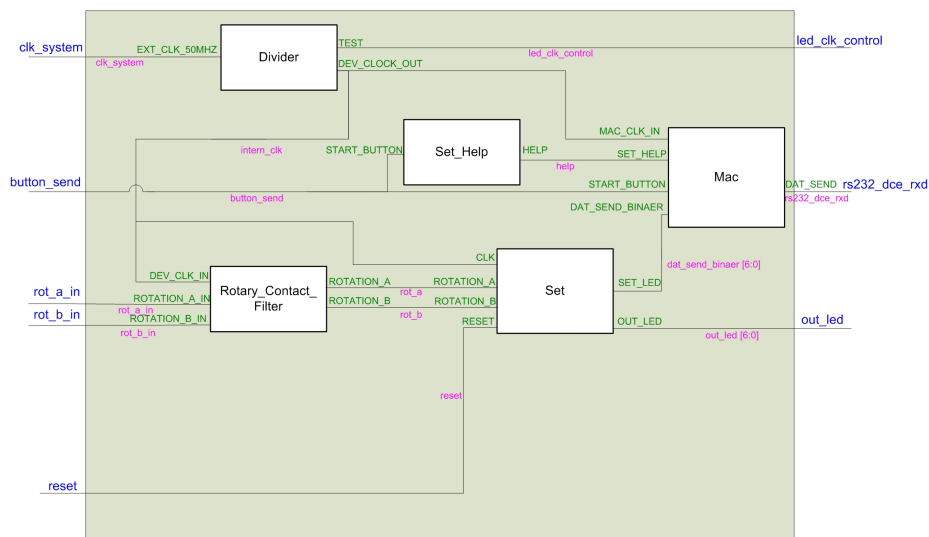


Abbildung 12: Signalverlaufplan: Senden mehrerer Zeichen





### 3.5.4 Konstante empfangen

Da die serielle Schnittstelle nicht nur senden sondern auch empfangen kann, sollte in diesem Projekt dieses verwirklicht werden. Dazu wurde das Eingangssignal 16-fach überabgetastet und eine Mehrheitsentscheidung programmiert. In jedem der 16 Werte pro empfangenem Bit wird der aktuelle Wert gespeichert. Besitzen mehr als 8 der 16 Werte „High“-Pegel, so wird dem Bit der Wert 1 zugeordnet, sonst 0.

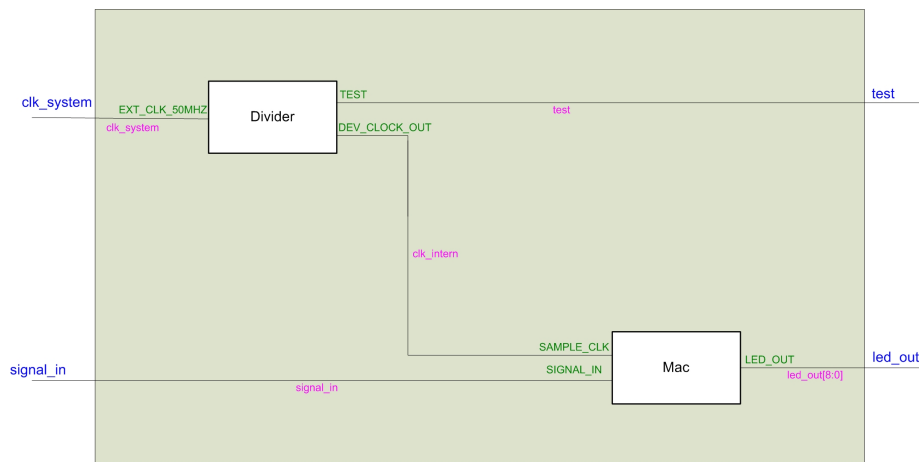


Abbildung 13: Signalverlaufplan: Konstante empfangen



### 3.5.5 Senden und Empfangen

#### Aufgabenstellung:

Verbinden der Sende- und Empfangsfunktion

#### Beschreibung:

In diesem Projekt wurde die Sende- und die Empfangsfunktion miteinander verknüpft. Es mussten zwei Instanzen von „Divider“ eingebunden werden, da das Abtasten des Eingangssignals eine 16-mal schnelleren Takt benötigt als das Senden. Beim Testen des Programms fiel auf, dass in unregelmäßigen Abständen zu sendende Bits anstatt 1 den Wert 0 oder umgekehrt annahmen. Dieser Fehler konnte behoben werden, indem in der Instanz „Mac“ die internen Signale zu Variablen umdeklariert wurden (Zeilen 26 bis 31). Variablen nehmen immer sofort den neuen Wert an und Signale ändern ihren Zustand erst beim Verlassen des Prozesses, also zum nächsten Takt.

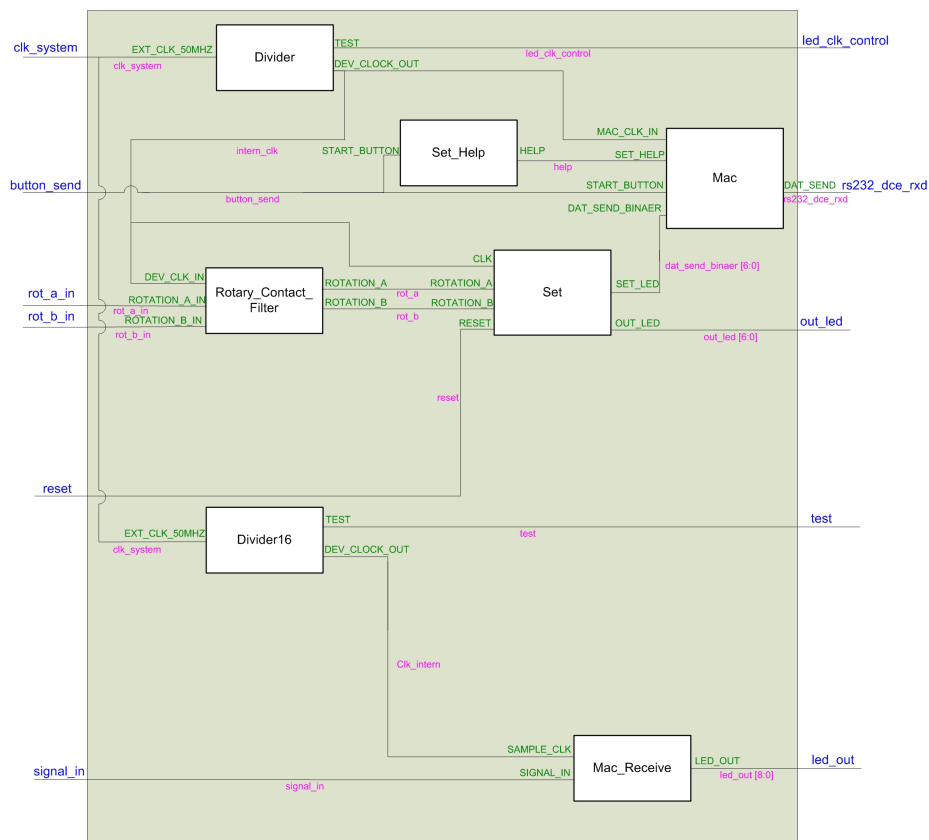


Abbildung 14: Signalverlaufplan: Senden und Empfangen



### 3.6 LC-Display

#### Aufgabenstellung:

LC-Display Initialisieren und Konstante ausgeben

#### Beschreibung:

Das LC-Display wird über die vier Signale „lcd\_dat“ (4 Bit Bus), „lcd\_e“, „lcd\_rw“ und „lcd\_rs“ gesteuert. Das Display reagiert auf steigende Flanken von Enable (lcd\_e). Durch die „when others“ Anweisung in Zeile 117 wird es immer wieder auf 0 zurückgesetzt. Liegt „lcd\_rw“ auf Low, handelt es sich um einen Schreibbefehl, sonst um einen Lesebefehl. „Lcd\_rs“ entscheidet ob Daten aus dem Statusregister oder aus dem Textpuffer ausgegeben werden. Vor der Inbetriebnahme des Displays muss eine Initialisierung (Abb.15) durchgeführt werden. Diese ist in der Instanz „Mac“ in den Zeilen 31 bis einschließlich 59 geschehen. Es folgt (Zeilen 60 bis 114) das Senden der Bitfolgen, die die Ausgabe steuern, diese entsprechen den Ascii-Zeichen (Abb. 16). Der Zähler „count“ sorgt dafür, dass die notwendigen Zeitabstände zwischen den einzelnen Befehlen eingehalten werden.

 


Abbildung 15: Initialisierung

Höhe 4 Tiefe 4 Bit	0010	0011	0100	0101	0110	0111
0000		0	@	P		p
0001	!	1	A	Q	a	q
0010	"	2	B	R	b	r
0011	#	3	C	S	c	s
0100	\$	4	D	T	d	t
0101	%	5	E	U	e	u
0110	&	6	F	V	f	v
0111	'	7	G	W	g	w
1000	(	8	H	X	h	x
1001	)	9	I	Y	i	y
1010	*	:	J	Z	j	z
1011	+	;	K	[	k	{
1100	,	<	L	¥	l	
1101	-	=	M	]	m	}
1110	.	>	N	^	n	→
1111	/	?	O	_	o	←

Abbildung 16: ASCII-Tabelle

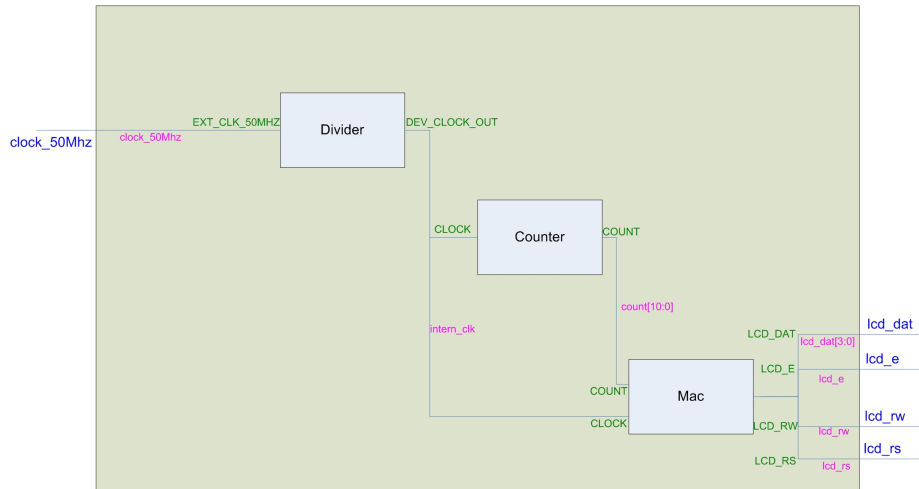


Abbildung 17: Signalverlaufplan: LC-Display

## 3.7 Vorverstärker

### 3.7.1 Verstärkung einstellen

#### Aufgabenstellung:

Vorverstärker ansteuern und Verstärkung einstellen

#### Beschreibung:

Der Vorverstärker regelt die Eingangsspannung des Analog-Digital-Wandlers auf Pegel, die den Bausteinparametern entsprechen.

Auf dem FPGA-Board sind zwei Ausgangspins mit Signalen belegt, die zum Analog-Digital-Wandler führen, die unterschiedlich verstärkt werden können. Angesteuert wird der Vorverstärker über den Serial-Peripheral-Interface-Bus (kurz: SPI-Bus).

Wie in Abbildung 18 dargestellt, mussten die drei Ausgangssignale „sck\_out“, „amp\_cs“ und „sdi“ geregelt werden. Das Signal „amp\_do“ ist ein Kontrollsignal, an dem abzulesen ist, was der Vorverstärker bei vorherigem Einstellen erkannt hat.

„Amp\_cs“ ist im „Ruhezustand“ immer auf high, sobald das Signal auf low wechselt ist der Baustein aktiv. Das Signal „sck\_out“ generiert 8 Clock-Takte mit der Periodendauer 100ns und auf „sdi“ wird die Bitfolge übertragen, die die Verstärkungen einstellt. Der nächste Wert des Signals „sdi“ wird angelgt, wenn das Taktsignal 25ns den Wert 0 hat, damit er bei der nächsten steigenden Flanke von „sck\_out“ anliegt.

Anschließend wird wieder der „Ruhezustand“ hergestellt, „amp\_cs“ wird wieder high, „sck\_out“ und „sdi“ wieder low.

Die Instanz „Set-Help“ stellt sicher, dass der Zähler „count“ der Instanz „Count\_Set\_Gain“ nur einmal durchlaufen wird.

 


Abbildung 18: Timing-Diagramm SPI

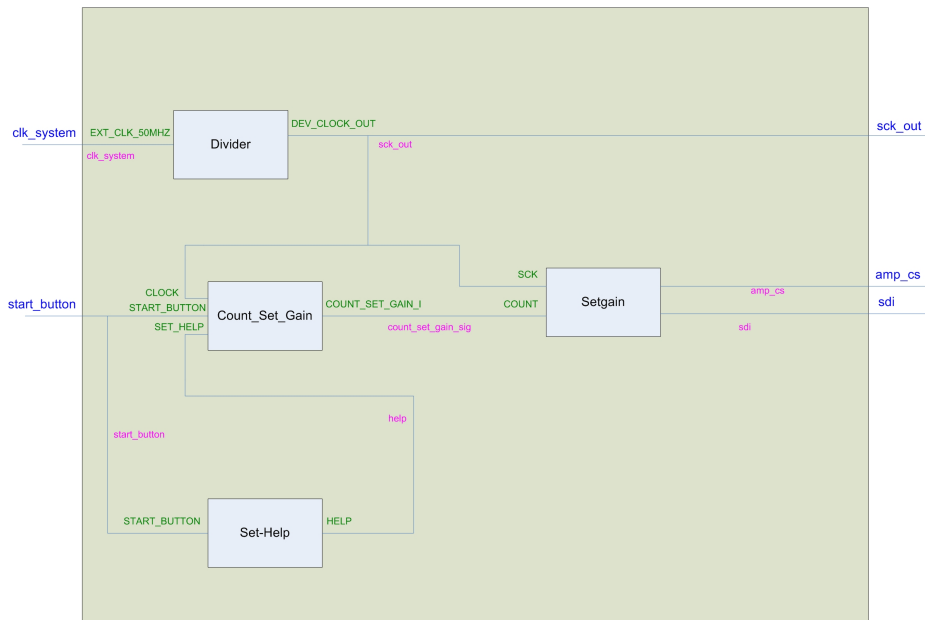


Abbildung 19: Signalverlaufplan: Verstärkung einstellen



### 3.7.2 Verstärkung anzeigen

#### Aufgabenstellung:

Verstärkungen einstellen und am LC-Display anzeigen

#### Beschreibung:

In diesem letzten Projekt wurden die beiden Projekte „LC-Display“ und „Verstärkung einstellen“ miteinander verbunden. Die eingestellte Verstärkung wird auf dem Display angezeigt (Abb. 20). Dafür wird in der Instanz „Setgain“ das Signal „amp\_do“ gelesen und in eine Bitfolge umgewandelt. Diese wird dann in der Instanz „Set\_gain\_z\_LCD“ umgeformt, sodass das LCD das Signal „verarbeiten“ kann und anschließend ausgeben kann. Die Initialisierung des LC-Displays und das Einstellen der Verstärkung sind gleich geblieben.



Abbildung 20: LC-Diplay

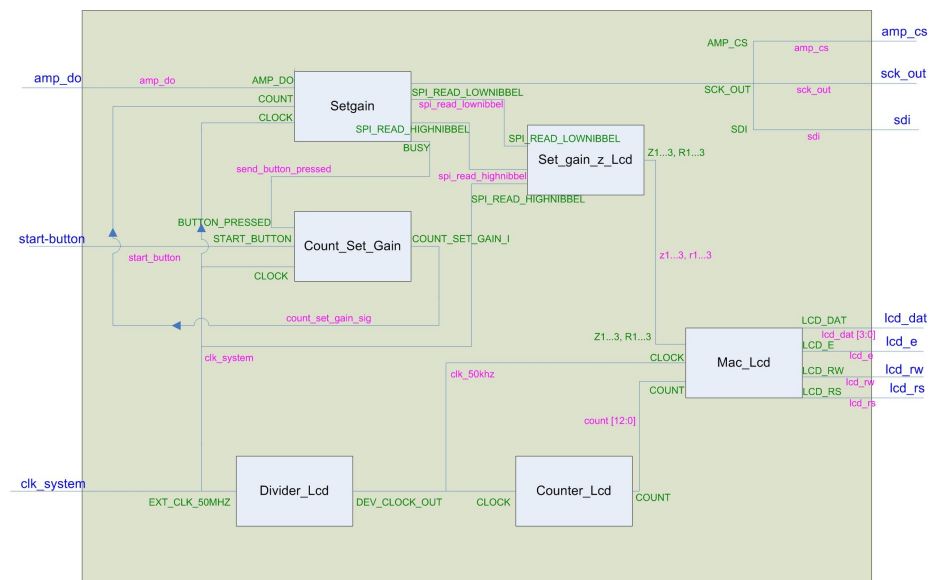


Abbildung 21: Signalverlaufplan: Verstärkung anzeigen



## 4 Zusammenfassung

Thema des Praxissemesters war die „ Inbetriebnahme eines Spartan 3E FPGA Evaluations Boards “. Zu dem FPGA Boards Spartan 3E der Firma Xilinx wurde die firmeneigene Entwicklungsumgebung ISE mitgeliefert, welches zur Programmentwicklung verwendet wurde .

Ziel des Praxissemesters war, sowohl für mich als auch für die betreuenden Ingenieure, einen Einblick in die Gebiete FPGA- und VHDL-Programmierung zu bekommen. Hierzu wurde nicht ein Großes, sondern viele kleine Projekte realisiert.

Nach einer kurzen Einarbeitung, in der geklärt wurde, was ein FPGA ist und wie man es programmiert, wurden die ersten Projekte verwirklicht.

Im Projekt „Takt teilen“ wurde der vom Evaluations Board gelieferte Takt von 50 MHz um einen beliebigen Faktor verringert. In „Ampelschaltung“ ging es primär um die Ansteuerung der LEDs und der Verknüpfung verschiedener Instanzen zu einem Projekt. Es folgte „Binär zählen“, hier wurde zum ersten Mal mit Vektoren gearbeitet und Taster verwendet. Als letztes Projekt das zum Block Einarbeitung gehörte, wurde „ Drehinkrementgeber“ programmiert. Dabei wurde der Drehinkrementgeber eingebunden und das Prellen unterdrückt.

Es folgten die drei Hauptaufgaben: das Programmieren der Schnittstelle EIA232, das Ansteuern des LC-Displays und das Einstellen des Vorverstärkers des Analog-Digital-Wandlers.

Über die Schnittstelle EIA232 (früher RS232) wurde zuerst schrittweise das Senden vom Board zum PC und anschließend das Empfangen von Daten vom PC umgesetzt.

Beim LC-Display war das Initialisieren des Displays die entscheidende Schwierigkeit, da es auf genaues Einhalten bestimmter Zeitabstände zwischen den einzelnen Initialisierungsbefehlen ankommt.

Als letzte Aufgabe wurde der Vorverstärker angesteuert. Hierbei wurde der Verstärkungsfaktor eingestellt, um den die Eingangsspannung verringert wurde. Dies wird zum Beispiel benötigt, damit am Analog-Digital-Wandler Signale ankommen, die seinen jeweiligen Bausteinparametern entspricht.



## A Anhang

### A.1 Takt teilen

```
led.vhd Wed Jun 18 10:51:59 2008
1  -----
2  --Projekt: Takt teilen
3  --Instanz: LED
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10 entity led is
11     Port ( clock : in  STD_LOGIC;
12           leds_out : inout STD_LOGIC_VECTOR (7 downto 0));
13 end led;
14
15 architecture Behavioral of led is
16 begin
17     process (clock)
18         variable divide_count : integer := 0;
19     begin
20         if rising_edge(clock) then
21             DIVIDE_COUNT := DIVIDE_COUNT + 1;
22             if DIVIDE_COUNT = 25000000 then
23                 LEDS_OUT(0) <= not LEDS_OUT(0);
24                 DIVIDE_COUNT := 0;
25             end if;
26         end if;
27     end process;
28
29 end Behavioral;
30
31
```






```
led.ucf                                     Wed Jun 18 10:52:16 2008
1      #-----
2      #--Projekt: Takt teilen
3      #--      User Constraint File
4      #-----
5
6
7      NET "clock"          LOC = "C9" ;
8      NET "leds_out<0>"   LOC = "F12" ;
9      NET "leds_out<1>"   LOC = "E12" ;
10     NET "leds_out<2>"   LOC = "E11" ;
11     NET "leds_out<3>"   LOC = "F11" ;
12     NET "leds_out<4>"   LOC = "C11" ;
13     NET "leds_out<5>"   LOC = "D11" ;
14     NET "leds_out<6>"   LOC = "E9" ;
15     NET "leds_out<7>"   LOC = "F9" ;
16
17
```



## A.2 Ampelschaltung

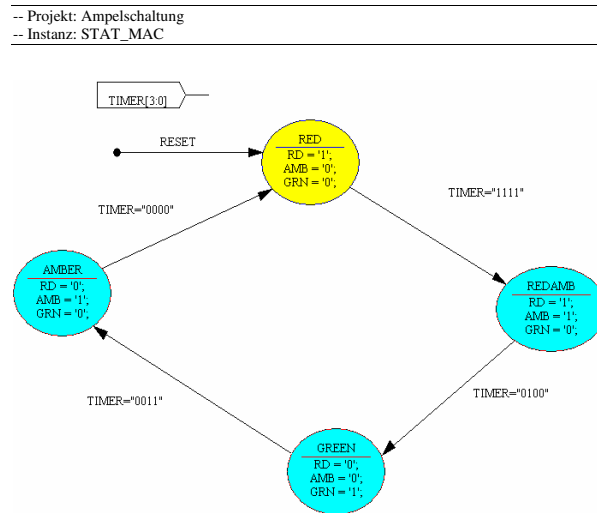



```
schem.vhd                                     Wed Jun 18 13:08:57 2008
1
2  -----
3  -- Copyright (c) 1995-2007 Xilinx, Inc. All rights reserved.
4  -----
5
6  --
7  -- Vendor: Xilinx
8  -- Version : 9.2i
9  -- Application : sch2vhdl
10 -- Filename : schem.vhf
11 -- Timestamp : 03/27/2008 16:13:50
12 --
13 --
14 --Command: D:\Programme\Xilinx92i\bin\nt\sch2vhdl.exe -intstyle ise -family spartan3e -f.
15 --suppress -w D:\Programme\Xilinx92i\test2\schem.sch schem.vhf
16 --Design Name: schem
17 --Device: spartan3e
18 --Purpose:
19 -- This vhdl netlist is translated from an ECS schematic. It can be
20 -- synthesis and simulated, but it should not be modified.
21 --
22
23 library ieee;
24 use ieee.std_logic_1164.ALL;
25 use ieee.numeric_std.ALL;
26 library UNISIM;
27 use UNISIM.Vcomponents.ALL;
28
29 entity schem is
30     port ( clk_in      : in    std_logic;
31           reset_in   : in    std_logic;
32           AMB        : inout std_logic;
33           GRN        : inout std_logic;
34           RD         : inout std_logic);
35 end schem;
36
37 architecture BEHAVIORAL of schem is
38     signal XLXN_61 : std_logic_vector (3 downto 0);
39     signal XLXN_674 : std_logic;
40     component Counter
41     port ( clock : in    std_logic;
42           reset : in    std_logic;
43           count : inout std_logic_vector (3 downto 0));
44     end component;
45
46     component divider
47     port ( ext_clk_50MHz : in    std_logic;
48           dev_clock_out : out   std_logic);
49     end component;
50
51     component STAT_MAC
52     port ( CLK : in    std_logic;
53           RESET : in    std_logic;
54           TIMER : in    std_logic_vector (3 downto 0);
55           AMB : out   std_logic;
56           GRN : out   std_logic;
57           RD : out   std_logic);
58     end component;
59
60 begin
61     XLXI_1 : Counter
```



```
schem.vhd Wed Jun 18 13:08:57 2008  
61     port map (clock=>XLXN_674,  
62               reset=>reset_in,  
63               count(3 downto 0)=>XLXN_61(3 downto 0));  
64  
65     XLXI_2 : divider  
66     port map (ext_clk_50MHz=>clk_in,  
67               dev_clock_out=>XLXN_674);  
68  
69     XLXI_3 : STAT_MAC  
70     port map (CLK=>XLXN_674,  
71               RESET=>reset_in,  
72               TIMER(3 downto 0)=>XLXN_61(3 downto 0),  
73               AMB=>AMB,  
74               GRN=>GRN,  
75               RD=>RD);  
76  
77     end BEHAVIORAL;  
78  
79  
80
```



```

top.vhd                                     Wed Jun 18 13:09:16 2008
1
2  -----
3  -- Projekt: Ampelschaltung
4  -- Instanz: TOP
5  -----
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12  entity top is
13      Port ( ext_clk_50MHz : in  STD_LOGIC;
14            reset         : in  STD_LOGIC;
15            red_light     : out  STD_LOGIC;
16            amber_light   : out  STD_LOGIC;
17            green_light   : out  STD_LOGIC;
18            dev_clock_out : inout STD_LOGIC
19          );
20  END entity top;
21
22  architecture Behavioral of top is
23      signal timer : std_logic_vector(3 downto 0);
24
25      COMPONENT counter
26      PORT(
27          CLOCK : IN std_logic;
28          RESET : IN std_logic;
29          COUNT : INOUT std_logic_vector(3 downto 0)
30        );
31      END COMPONENT;
32
33      COMPONENT stat_mac
34      PORT (
35          TIMER : IN std_logic_vector(3 downto 0);
36          CLK   : IN std_logic;
37          RESET : IN std_logic;
38          AMB   : OUT std_logic;
39          GRN   : OUT std_logic;
40          RD    : OUT std_logic
41        );
42      END COMPONENT;
43
44      COMPONENT divider
45      PORT (
46          ext_clk_50MHz : in  STD_LOGIC;
47          dev_clock_out : out  STD_LOGIC
48        );
49      end COMPONENT;
50
51  begin
52      Inst_counter: counter PORT MAP
53      (
54          CLOCK => dev_clock_out,
55          RESET => reset,
56          COUNT => timer
57      );
58
59
60      Inst_stat_mac: stat_mac PORT MAP
61      (

```



```
top.vhd Wed Jun 18 13:09:16 2008  
62     TIMER => timer,  
63     CLK  => dev_clock_out,  
64     RESET => reset,  
65     AMB  => amber_light,  
66     GRN  => green_light,  
67     RD   => red_light  
68     );  
69  
70     Inst_divider: divider PORT MAP (  
71         ext_clk_50MHz => ext_clk_50MHz,  
72         dev_clock_out => dev_clock_out  
73     );  
74  
75     end Behavioral;
```



```
divider.vhd                                     Wed Jun 18 13:09:28 2008
1  -----
2  --Projekt: Ampelschaltung
3  --Instanz: Divider
4  -----
5
6
7  library IEEE;
8  use IEEE.STD_LOGIC_1164.ALL;
9  use IEEE.STD_LOGIC_ARITH.ALL;
10 use IEEE.STD_LOGIC_UNSIGNED.ALL;
11
12
13
14 entity divider is
15   Port (
16     ext_clk_50MHz : in  STD_LOGIC;
17     dev_clock_out : inout STD_LOGIC -- 2Hz
18   );
19 end divider;
20
21
22 architecture Behavioral of divider is
23   signal divide_counter : integer := 0;
24
25 begin
26
27   Process(ext_clk_50MHz)
28   begin
29     if (rising_edge (ext_clk_50MHz)) then
30       if (divide_counter /= 12500000) then
31         divide_counter <= divide_counter + 1;
32       else
33         divide_counter <= 0;
34         dev_clock_out <= not (dev_clock_out);
35       end if;
36     end if;
37   end process;
38 end Behavioral;
```



```
Counter.vhd                                     Wed Jun 18 13:09:34 2008
1  -----
2  --Projekt: Ampelschaltung
3  --Instanz: Counter
4  -----
5
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10 -----Berechnet den zustand der Ampel
11
12 entity Counter is
13     Port ( clock : in  STD_LOGIC;
14           reset : in  STD_LOGIC;
15           count : inout STD_LOGIC_VECTOR (3 downto 0));
16 end Counter;
17
18 architecture Behavioral of Counter is
19
20 begin
21 process (clock, reset)
22     begin
23         if reset='1' then
24             count <= "0000";
25         elsif clock='1' and clock'event then
26             count <= count + 1;
27         end if;
28     end process;
29 end Behavioral;
```





```
schem.ucf                                     Wed Jun 18 13:09:41 2008
1  #-----
2  #Projekt: Ampelschaltung
3  #   User Constraint File
4  #-----
5  NET "amber_light"   LOC = "E12"  ;
6  NET "ext_clk_50MHz" LOC = "C9"   ;
7  NET "green_light"  LOC = "F12"  ;
8  NET "red_light"    LOC = "E11"  ;
9  NET "reset"        LOC = "K17"  ;
10 NET "dev_clock_out" LOC = "F9"  ;
11
12
```



## A.3 Binär zählen

```

top.vhd                                     Wed Jun 18 13:20:05 2008
1  -----
2  --Projekt: Binär zählen
3  --Instanz: Top
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity top is
13      Port ( SOUTH      : in  STD_LOGIC;
14            WEST       : in  STD_LOGIC;
15            EAST       : in  STD_LOGIC;
16            S_0        : in  STD_LOGIC; -- Schalter
17            S_1        : in  STD_LOGIC; -- Schalter
18            S_2        : in  STD_LOGIC; -- Schalter
19            LED        : inout STD_LOGIC_VECTOR (2 downto 0);
20            clk_system : in  STD_LOGIC;
21            intern_clk : inout STD_LOGIC
22        );
23
24  end top;
25
26  architecture Behavioral of top is
27
28  COMPONENT divider
29      PORT (
30          ext_clk_50MHz : in  STD_LOGIC;
31          dev_clock_out : inout STD_LOGIC
32      );
33  end COMPONENT;
34
35  COMPONENT mac
36      PORT (
37          SOUTH      : in  STD_LOGIC;
38          WEST       : in  STD_LOGIC;
39          EAST       : in  STD_LOGIC;
40          S_0        : in  STD_LOGIC; -- Schalter
41          S_1        : in  STD_LOGIC; -- Schalter
42          S_2        : in  STD_LOGIC; -- Schalter
43          LED        : inout STD_LOGIC_VECTOR (2 downto 0);
44          dev_clock_out : in  STD_LOGIC
45      );
46  end COMPONENT;
47
48  begin
49
50  Inst_divider: divider PORT MAP
51      (
52          ext_clk_50MHz => clk_system,
53          dev_clock_out => intern_clk
54      );
55
56  Inst_mac: mac PORT MAP
57      (
58          dev_clock_out => intern_clk,
59          SOUTH        => SOUTH,
60          WEST         => West,
61          EAST         => EAST,
62          S_0          => S_0,

```



```
top.vhd                                     Wed Jun 18 13:20:05 2008
62             S_1             => S_1,
63             S_2             => S_2,
64             LED             => LED
65         );
66     end Behavioral;
67
68
```



```
MAC.vhd                                     Wed Jun 18 13:20:15 2008
1  -----
2  --Projekt: Binär Zählen
3  --Instanz: Mac
4  -----
5
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11  entity MAC is
12      Port ( SOUTH      : in  STD_LOGIC;
13            EAST       : in  STD_LOGIC;
14            WEST       : in  STD_LOGIC;
15            S_0        : in  STD_LOGIC;
16            S_1        : in  STD_LOGIC;
17            S_2        : in  STD_LOGIC;
18            LED        : inout STD_LOGIC_VECTOR (2 downto 0);
19            dev_clock_out : in  STD_LOGIC
20          );
21  end MAC;
22
23  architecture Behavioral of MAC is
24
25  begin
26
27
28  process (WEST,SOUTH,EAST,S_0,S_1,S_2,dev_clock_out)
29  begin
30      if East='1' then          -- reset
31          LED <= "000";
32      elsif rising_edge(dev_clock_out) then
33          if SOUTH='1' then
34              LED <= LED + 1;
35          elsif WEST='1' then
36              LED <= LED - 1;
37          elsif S_0='1'
38              then LED(0) <= not LED (0);
39          elsif S_1='1'
40              then LED(1) <= not LED (1);
41          elsif S_2='1'
42              then LED(2) <= not LED (2);
43          end if;
44      end if;
45  end process;
46
47  end Behavioral;
```



```
DIVIDER.vhd Wed Jun 18 13:20:24 2008
1  -----
2  --Projekt: Binär Zählen
3  --Instanz: Divider
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity divider is
13  port (
14      ext_clk_50MHz : in    STD_LOGIC;
15      dev_clock_out : inout STD_LOGIC
16  );
17  end divider;
18
19
20  architecture Behavioral of divider is
21  signal divide_counter : integer := 0;
22
23
24  begin
25
26  Process(ext_clk_50MHz)
27  begin
28      if (rising_edge (ext_clk_50MHz)) then
29          if (divide_counter /= 2600) then
30              divide_counter <= divide_counter + 1;
31          else
32              divide_counter <= 0;
33              dev_clock_out <= not ( dev_clock_out);
34          end if;
35      end if;
36  end process;
37  end Behavioral;
```



```
top.ucf                                     Wed Jun 18 13:20:32 2008
1      #-----
2      #Projekt: Binär Zählen
3      # User Constraint File
4      #-----
5      NET "clk_system" LOC = "C9" ;
6      NET "EAST" LOC = "H13" ;
7      NET "LED<0>" LOC = "F12" ;
8      NET "LED<1>" LOC = "E12" ;
9      NET "LED<2>" LOC = "E11" ;
10     NET "S_0" LOC = "L13" ;
11     NET "S_1" LOC = "L14" ;
12     NET "S_2" LOC = "H18" ;
13     NET "SOUTH" LOC = "K17" ;
14     NET "WEST" LOC = "D18" ;
15
16
```



## A.4 Drehinkrementgeber

```

top.vhd                                     Wed Jun 18 13:32:04 2008
1
2  -----
3  --Projekt: Drehinkrementgeber
4  --Instanz: Top
5  -----
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11  entity top is
12  Port ( rotation_b_in : in  STD_LOGIC;
13        rotation_a_in : in  STD_LOGIC;
14        reset         : in  STD_LOGIC;
15        clk_system    : in  STD_LOGIC;
16        test          : out  STD_LOGIC;
17        direction     : inout STD_LOGIC_VECTOR (1 downto 0);
18        position      : inout STD_LOGIC_VECTOR (4 downto 0)
19  );
20  end top;
21
22  architecture Behavioral of top is
23
24  signal rotation_a : STD_LOGIC;
25  signal rotation_b : STD_LOGIC;
26  signal intern_clk : STD_LOGIC;
27
28  COMPONENT mac PORT ( rotation_b : in  STD_LOGIC;
29                      rotation_a : in  STD_LOGIC;
30                      reset      : in  STD_LOGIC;
31                      test       : out  STD_LOGIC;
32                      direction  : inout STD_LOGIC_VECTOR (1 downto 0);
33                      position   : inout STD_LOGIC_VECTOR (4 downto 0)
34  );
35  end COMPONENT;
36
37  COMPONENT rotary_contact_filter PORT
38  (
39      rotation_a_in : in  STD_LOGIC;
40      rotation_b_in : in  STD_LOGIC;
41      dev_clk_in   : in  STD_LOGIC;
42      rotation_a   : inout STD_LOGIC;
43      rotation_b   : inout STD_LOGIC
44  );
45  end COMPONENT;
46
47  COMPONENT DIVIDER PORT
48  (
49      ext_clk_50MHz : in  STD_LOGIC;
50      test          : out  STD_LOGIC;
51      dev_clock_out : inout STD_LOGIC
52  );
53  end COMPONENT;
54
55  begin
56  Inst_DIVIDER: DIVIDER PORT MAP
57  (
58      ext_clk_50MHz => clk_system,
59      dev_clock_out => intern_clk,
60      test         => test
61  );

```



```
top.vhd                                     Wed Jun 18 13:32:04 2008
62
63     Inst_rotary_contact_filter: rotary_contact_filter PORT MAP
64     (
65         rotation_a_in => rotation_a_in,
66         rotation_b_in => rotation_b_in,
67         dev_clk_in    => intern_clk,
68         rotation_a    => rotation_a,
69         rotation_b    => rotation_b
70     );
71
72
73
74     Inst_mac: mac PORT MAP
75     (
76         position  => position,
77         rotation_a => rotation_a,
78         rotation_b => rotation_b,
79         direction => direction,
80         reset     => reset
81     );
82 end Behavioral;
83
84
```





```
mac.vhd                                     Wed Jun 18 13:32:11 2008
1  -----
2  --Projekt: Drehinkrementgeber
3  --Instanz: Mac
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10 entity mac is
11     Port ( rotation_b      : in  STD_LOGIC;
12           rotation_a      : in  STD_LOGIC;
13           reset           : in  STD_LOGIC;
14           test            : out STD_LOGIC;
15           direction       : out STD_LOGIC_VECTOR (1 downto 0);
16           position        : inout STD_LOGIC_VECTOR (4 downto 0)
17     );
18 end mac;
19
20 architecture Behavioral of mac is
21 begin
22 process (reset, rotation_a, rotation_b)
23 begin
24 if reset='1' then
25     position <= "00000";
26 elsif rising_edge(rotation_a) then
27     if rotation_b = '1' then
28         direction <= "10";
29         position <= position -1;
30     else direction <= "01";
31         position <= position +1;
32     end if;
33
34 end if;
35 end process;
36 end Behavioral;
```



```
Rotary_contact_filter.vhd                                     Wed Jun 18 13:32:19 2008
1  -----
2  --Projekt: Drehinkrementgeber
3  --Instanz: rotary_contact_filter
4  -----
5
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12  entity rotary_contact_filter is
13  port ( rotation_a_in : in  STD_LOGIC;
14        rotation_b_in : in  STD_LOGIC;
15        dev_clk_in    : in  STD_LOGIC;
16        rotation_a    : inout STD_LOGIC;
17        rotation_b    : inout STD_LOGIC
18        );
19  end rotary_contact_filter;
20
21  architecture Behavioral of rotary_contact_filter is
22  signal rotation_in : STD_LOGIC_VECTOR (1 downto 0);
23  begin
24  process(dev_clk_in)
25  begin
26  if (rising_edge(dev_clk_in)) then
27  rotation_in <= rotation_b_in & rotation_a_in;
28  case rotation_in is
29  when "00" => rotation_a <= '0';
30  rotation_b <= rotation_b;
31  when "01" => rotation_a <= rotation_a;
32  rotation_b <= '0';
33  when "10" => rotation_a <= rotation_a;
34  rotation_b <= '1';
35  when "11" => rotation_a <= '1';
36  rotation_b <= rotation_b;
37  when others => rotation_a <= rotation_a;
38  rotation_b <= rotation_b;
39  end case;
40  end if;
41  end process;
42
43  end Behavioral;
```



```
DIVIDER.vhd                                     Wed Jun 18 13:32:25 2008
1  -----
2  --Projekt: Drehinkrementgeber
3  --Instanz: Divider
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity divider is
13  port (
14      ext_clk_50MHz : in    STD_LOGIC;
15      dev_clock_out : inout STD_LOGIC
16  );
17  end divider;
18
19
20  architecture Behavioral of divider is
21  signal divide_counter : integer := 0;
22
23
24  begin
25
26  Process(ext_clk_50MHz)
27  begin
28      if (rising_edge (ext_clk_50MHz)) then
29          if (divide_counter /= 2500) then
30              divide_counter <= divide_counter + 1;
31          else
32              divide_counter <= 0;
33              dev_clock_out <= not ( dev_clock_out);
34          end if;
35      end if;
36  end process;
37  end Behavioral;
```



```
top.ucf 1 / 1  
#-----  
# Projekt: Drehinkrementgeber  
# User Constraint File  
#-----  
NET "clk_system" LOC = "C9" ;  
NET "direction<0>" LOC = "F12" ;  
NET "direction<1>" LOC = "E12" ;  
NET "position<0>" LOC = "F11" ;  
NET "position<1>" LOC = "C11" ;  
NET "position<2>" LOC = "D11" ;  
NET "position<3>" LOC = "E9" ;  
NET "position<4>" LOC = "F9" ;  
NET "reset" LOC = "V16" |PULLDOWN ;  
NET "rotation_a_in" LOC = "K18" |PULLUP ;  
NET "rotation_b_in" LOC = "G18" |PULLUP ;  
NET "test" LOC = "E11" ;
```



## A.5 Konstante senden

```

TOP.vhd                                     Wed Jun 25 14:12:03 2008
1  -----
2  -- Projekt: Konstante senden
3  -- Instanz: Top
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity TOP is
13      PORT (
14          clk_system      : in  STD_LOGIC;
15          button_send     : in  STD_LOGIC;
16          intern_clk      : inout STD_LOGIC;
17          RS232_DCE_RXD   : out  STD_LOGIC
18      );
19  end TOP;
20
21
22
23  architecture Behavioral of TOP is
24      COMPONENT divider
25          PORT (
26              ext_clk_50MHz : in  STD_LOGIC;
27              dev_clock_out : inout STD_LOGIC
28          );
29  end COMPONENT;
30
31      COMPONENT MAC
32          PORT (
33              dat_send      : out  STD_LOGIC;
34              mac_clk_in    : in  STD_LOGIC;
35              start_button  : in  STD_LOGIC
36          );
37  end COMPONENT;
38  begin
39
40      Inst_divider: divider PORT MAP
41          (
42              ext_clk_50MHz => clk_system,
43              dev_clock_out => intern_clk
44          );
45
46      Inst_mac: mac PORT MAP
47          (
48              dat_send      => RS232_DCE_RXD,
49              mac_clk_in    => intern_clk,
50              start_button  => button_send
51          );
52  end Behavioral;
53
54

```



```
MAC.vhd                                     Wed Jun 25 14:12:18 2008
1  -----
2  -- Projekt: Konstante senden
3  -- Instanz: Mac
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity MAC is
13  port(
14      dat_send      : out STD_LOGIC;
15      start_button : in  STD_LOGIC;
16      mac_clk_in   : in  STD_LOGIC
17  );
18  end MAC;
19
20  architecture Behavioral of MAC is
21
22  signal dat_send_complete : STD_LOGIC_VECTOR (9 downto 0) := "1111110110";
23  signal counter_index     : integer ;
24  signal help: integer := 0;
25
26  begin
27  process (mac_clk_in, start_button)
28  begin
29
30  if rising_edge (mac_clk_in) THEN
31  if start_button = '1' THEN
32  if help = 0 then
33  if counter_index < 10 THEN
34  counter_index <= counter_index + 1;
35  dat_send <= dat_send_complete(counter_index);
36  help <= 0;
37  else counter_index <= 0;
38  help <= 1;
39  end if;
40  end if;
41  elsif start_button = '0' THEN
42  if help = 0 Then
43  if counter_index > 0 THEN
44  if Counter_index < 10 THEN
45  counter_index <= counter_index + 1;
46  dat_send <= dat_send_complete(counter_index);
47  else Counter_index <= 0;
48  help <= 1;
49  end if;
50  end if;
51  end if;
52  end if;
53  end process;
54  end Behavioral;
```



```
DIVIDER.vhd                                     Wed Jun 25 14:12:54 2008
1  -----
2  --Projekt: Konstante Senden
3  --Instanz: Divider
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity divider is
13  port (
14      ext_clk_50MHz : in    STD_LOGIC;
15      dev_clock_out : inout STD_LOGIC
16  );
17  end divider;
18
19
20  architecture Behavioral of divider is
21  signal divide_counter : integer := 0;
22
23
24  begin
25
26  Process(ext_clk_50MHz)
27  begin
28      if (rising_edge(ext_clk_50MHz)) then
29          if (divide_counter /= 2500) then
30              divide_counter <= divide_counter + 1;
31          else
32              divide_counter <= 0;
33              dev_clock_out <= not (dev_clock_out);
34          end if;
35      end if;
36  end process;
37  end Behavioral;
```



```
TOP.ucf                                     Wed Jun 25 14:13:06 2008
1      #-----
2      # Projekt: Konstante senden
3      #   User Constraint File
4      #-----
5      NET "button_send"      LOC = "R17";
6      NET "clk_system"      LOC = "C9";
7      NET "intern_clk"      LOC = "E12";
8      NET "RS232_DCE_RXD"   LOC = "M14";
9      INST "Inst_mac/dat_send"      INIT = 1;
```





## A.6 Variable senden

```

TOP.vhd
-----
1
2
3 --Projekt: Variable senden
4 --Instanz: Top
5 -----
6 library IEEE;
7 use IEEE.STD_LOGIC_1164.ALL;
8 use IEEE.STD_LOGIC_ARITH.ALL;
9 use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11 entity TOP is
12     PORT (
13         clk_system      : in   STD_LOGIC;
14         rot_a_in        : in   STD_LOGIC;
15         rot_b_in        : in   STD_LOGIC;
16         reset           : in   STD_LOGIC;
17         button_send     : in   STD_LOGIC;
18         led_clk_control : out  STD_LOGIC;
19         set_led         : inout STD_LOGIC_VECTOR (6 downto 0);
20         out_led         : out  STD_LOGIC_VECTOR (6 downto 0);
21         RS232_DCE_RXD   : out  STD_LOGIC
22     );
23
24 end TOP;
25
26 architecture Behavioral of TOP is
27
28     signal rot_a          : STD_LOGIC;
29     signal rot_b          : STD_LOGIC;
30     signal dat_send_binaer : STD_LOGIC_VECTOR (6 downto 0);
31     signal intern_clk     : STD_LOGIC;
32
33     COMPONENT divider
34     PORT (
35         ext_clk_50MHz      : in   STD_LOGIC;
36         test               : out  STD_LOGIC;
37         dev_clock_out     : inout STD_LOGIC
38     );
39 end COMPONENT;
40
41     COMPONENT MAC
42     PORT(
43         dat_send          : out  STD_LOGIC;
44         start_button     : in   STD_LOGIC;
45         dat_send_binaer  : in   STD_LOGIC_VECTOR (6 downto 0);
46         mac_clk_in       : in   STD_LOGIC
47     );
48 end COMPONENT;
49
50     COMPONENT rotary_contact_filter
51     Port ( rotation_a_in : in   STD_LOGIC;
52           rotation_b_in : in   STD_LOGIC;
53           dev_clk_in    : in   STD_LOGIC;
54           rotation_a    : inout STD_LOGIC;
55           rotation_b    : inout STD_LOGIC
56     );
57 end COMPONENT;
58
59     COMPONENT set
60     PORT ( rotation_a : in STD_LOGIC;
61           rotation_b : in STD_LOGIC;

```



```
TOP.vhd                                     Wed Jun 18 13:55:31 2008
62      clk      : in STD_LOGIC;
63      reset   : in STD_LOGIC;
64      out_led  : out STD_LOGIC_VECTOR (6 downto 0);
65      set_led  : inout STD_LOGIC_VECTOR (6 downto 0)
66      );
67  end COMPONENT;
68  begin
69
70  Inst_divider: divider PORT MAP
71  (
72      ext_clk_50MHz => clk_system,
73      test         => led_clk_control,
74      dev_clock_out => intern_clk
75  );
76
77  Inst_mac: mac PORT MAP
78  (
79      dat_send      => RS232_DCE_RXD,
80      mac_clk_in    => intern_clk,
81      start_button  => button_send,
82      dat_send_binaer => dat_send_binaer
83  );
84
85  Inst_rotary_contact_filter: rotary_contact_filter PORT MAP
86  (
87      rotation_a_in => rot_a_in,
88      rotation_b_in => rot_b_in,
89      dev_clk_in    => intern_clk,
90      rotation_a    => rot_a,
91      rotation_b    => rot_b
92  );
93
94  Inst_set: set PORT MAP
95  (
96      rotation_a    => rot_a,
97      rotation_b    => rot_b,
98      clk           => intern_clk,
99      out_led       => out_led,
100     reset         => reset,
101     set_led        => dat_send_binaer
102  );
103
104  end Behavioral;
```



```
MAC.vhd                                     Wed Jun 18 13:55:40 2008
1  -----
2  --Projekt: Variable senden
3  --Instanz: Mac
4  -----
5
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12  entity MAC is
13  port(
14      dat_send          : out STD_LOGIC;
15      start_button     : in  STD_LOGIC;
16      dat_send_binaer  : in  STD_LOGIC_VECTOR (6 downto 0);
17      mac_clk_in       : in  STD_LOGIC
18  );
19  end MAC;
20
21  architecture Behavioral of MAC is
22
23  signal counter_index : integer ;
24  signal help          : integer := 0;
25  signal dat_send_complete : STD_LOGIC_VECTOR (9 downto 0);
26
27  begin
28  process (mac_clk_in)
29  begin
30  if rising_edge (mac_clk_in) then
31
32      dat_send_complete(9) <= '1';
33      dat_send_complete(8) <= '1';
34      dat_send_complete(7) <= dat_send_binaer(6);
35      dat_send_complete(6) <= dat_send_binaer(5);
36      dat_send_complete(5) <= dat_send_binaer(4);
37      dat_send_complete(4) <= dat_send_binaer(3);
38      dat_send_complete(3) <= dat_send_binaer(2);
39      dat_send_complete(2) <= dat_send_binaer(1);
40      dat_send_complete(1) <= dat_send_binaer(0);
41      dat_send_complete(0) <= '0';
42  end if;
43  end process;
44
45
46  process (mac_clk_in)
47  begin
48
49  if rising_edge (mac_clk_in) THEN
50  if start_button = '1' THEN
51  if help = 0 then
52  if counter_index < 10 THEN
53  counter_index <= counter_index + 1;
54  dat_send <= dat_send_complete(counter_index);
55  help <= 0;
56  else counter_index <= 0;
57  help <= 1;
58  end if;
59  end if;
60  elsif start_button = '0' THEN
```



```
MAC.vhd Wed Jun 18 13:55:40 2008  
62     if help = 0 Then  
63         if counter_index > 0 THEN  
64             if Counter_index < 10 THEN  
65                 counter_index <= counter_index + 1;  
66                 dat_send <= dat_send_complete(counter_index);  
67             else Counter_index <= 0;  
68                 help <= 1;  
69             end if;  
70         end if;  
71     end if;  
72 end if;  
73 end process;  
74 end process;  
75 end Behavioral;
```



```
FILTER.vhd                                     Wed Jun 18 13:55:48 2008
1  -----
2  --Projekt: Variable senden
3  --Instanz: Rotary_Contact_Filter
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity rotary_contact_filter is
13  port ( rotation_a_in : in   STD_LOGIC;
14        rotation_b_in : in   STD_LOGIC;
15        dev_clk_in    : in   STD_LOGIC;
16        rotation_a    : inout STD_LOGIC;
17        rotation_b    : inout STD_LOGIC
18  );
19  end rotary_contact_filter;
20
21  architecture Behavioral of rotary_contact_filter is
22  signal rotation_in : STD_LOGIC_VECTOR (1 downto 0);
23  begin
24  process(dev_clk_in)
25  begin
26  if (rising_edge (dev_clk_in)) then
27  rotation_in <= rotation_b_in & rotation_a_in;
28  case rotation_in is
29  when "00" => rotation_a <= '0';
30  rotation_b <= rotation_b;
31  when "01" => rotation_a <= rotation_a;
32  rotation_b <= '0';
33  when "10" => rotation_a <= rotation_a;
34  rotation_b <= '1';
35  when "11" => rotation_a <= '1';
36  rotation_b <= rotation_b;
37  when others => rotation_a <= rotation_a;
38  rotation_b <= rotation_b;
39  end case;
40  end if;
41  end process;
42  end Behavioral;
43
```



```
SET.vhd                                     Wed Jun 18 13:55:57 2008
1  -----
2  --Projekt: Variable senden
3  --Instanz: SET
4  -----
5
6
7  library IEEE;
8  use IEEE.STD_LOGIC_1164.ALL;
9  use IEEE.STD_LOGIC_ARITH.ALL;
10 use IEEE.STD_LOGIC_UNSIGNED.ALL;
11
12 -----
13 ---DREHGEBER-->LEDS_SETZEN---
14 -----
15
16
17 entity SET is
18     PORT ( rotation_a : in STD_LOGIC;
19           rotation_b : in STD_LOGIC;
20           reset       : in STD_LOGIC;
21           out_led     : out STD_LOGIC_VECTOR (6 downto 0);
22           clk         : in STD_LOGIC;
23           set_led     : inout STD_LOGIC_VECTOR (6 downto 0)
24           );
25
26 end SET;
27
28 architecture Behavioral of SET is
29 begin
30
31 process (reset, rotation_a, rotation_b)
32 begin
33     if reset='1' then
34         set_led <= "00000000";
35     elsif rising_edge(rotation_a) then
36         if rotation_b='1' then
37             set_led <= set_led -1;
38             else set_led <= set_led +1;
39         end if;
40     end if;
41 end process;
42
43 process (clk)
44 begin
45     if rising_edge(clk) then
46         out_led(6) <= set_led(6);
47         out_led(5) <= set_led(5);
48         out_led(4) <= set_led(4);
49         out_led(3) <= set_led(3);
50         out_led(2) <= set_led(2);
51         out_led(1) <= set_led(1);
52         out_led(0) <= set_led(0);
53     end if;
54 end process;
55 end Behavioral;
56
57
58
```



```
divider.vhd                                     Wed Jun 18 13:56:05 2008
1  -----
2  --Projekt: Variable senden
3  --Instanz: Divider
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity divider is
13  port (
14      ext_clk_50MHz      : in      STD_LOGIC;
15      test               : out    STD_LOGIC;
16      dev_clock_out     : inout   STD_LOGIC
17  );
18  end divider;
19
20
21  architecture Behavioral of divider is
22  signal divide_counter : integer := 0;
23
24  begin
25
26  Process(ext_clk_50MHz)
27  begin
28      if (rising_edge (ext_clk_50MHz)) then
29          if (divide_counter /= 2600) then
30              divide_counter <= divide_counter + 1;
31          else
32              divide_counter <= 0;
33              dev_clock_out <= not (dev_clock_out);
34              test <= dev_clock_out ;
35          end if;
36      end if;
37  end process;
38  end Behavioral;
39
40
41
```



```
TOP.ucf                                     Wed Jun 18 13:56:15 2008
1      #-----
2      #Projekt: Variable senden
3      # User Constraint File
4      #-----
5      NET "button_send"      LOC = "K17" ;
6      NET "clk_system"      LOC = "C9"  ;
7      NET "led_clk_control"  LOC = "F12" ;
8      NET "out_led<0>"      LOC = "E12" ;
9      NET "out_led<1>"      LOC = "E11" ;
10     NET "out_led<2>"      LOC = "F11" ;
11     NET "out_led<3>"      LOC = "C11" ;
12     NET "out_led<4>"      LOC = "D11" ;
13     NET "out_led<5>"      LOC = "E9"  ;
14     NET "out_led<6>"      LOC = "F9"  ;
15     NET "rot_a_in"         LOC = "K18" | PULLUP ;
16     NET "rot_b_in"         LOC = "G18" | PULLUP ;
17     NET "RS232_DCE_RXD"    LOC = "M14" ;
18     NET "reset"           LOC = "V16" | PULLDOWN ;
19     INST "Inst_mac/dat_send"          INIT = 1;
20
21
```





## A.7 Senden mehrerer Zeichen

```

TOP.vhd                                     Wed Jun 18 14:33:08 2008
1  -----
2  --Projekt: Senden mehrerer Zeichen
3  --Instanz: Top
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11  entity TOP is
12      PORT (
13          clk_system      : in   STD_LOGIC;
14          rot_a_in        : in   STD_LOGIC;
15          rot_b_in        : in   STD_LOGIC;
16          reset           : in   STD_LOGIC;
17          button_send     : in   STD_LOGIC;
18          led_clk_control : out  STD_LOGIC;
19          set_led         : inout STD_LOGIC_VECTOR (6 downto 0);
20          out_led         : out  STD_LOGIC_VECTOR (6 downto 0);
21          RS232_DCE_RXD   : out  STD_LOGIC
22      );
23
24  end TOP;
25
26  architecture Behavioral of TOP is
27
28      signal rot_a          : STD_LOGIC;
29      signal rot_b          : STD_LOGIC;
30      signal dat_send_binaer : STD_LOGIC_VECTOR (6 downto 0);
31      signal intern_clk     : STD_LOGIC;
32      signal help           : STD_LOGIC;
33
34      COMPONENT divider
35      PORT (
36          ext_clk_50MHz     : in   STD_LOGIC;
37          test              : out  STD_LOGIC;
38          dev_clock_out    : inout STD_LOGIC
39      );
40  end COMPONENT;
41
42      COMPONENT MAC
43      PORT(
44          dat_send          : out  STD_LOGIC;
45          start_button      : in   STD_LOGIC;
46          dat_send_binaer   : in   STD_LOGIC_VECTOR (6 downto 0);
47          set_help         : inout STD_LOGIC;
48          mac_clk_in       : in   STD_LOGIC
49      );
50  end COMPONENT;
51
52      COMPONENT rotary_contact_filter
53      Port ( rotation_a_in : in   STD_LOGIC;
54            rotation_b_in : in   STD_LOGIC;
55            dev_clk_in    : in   STD_LOGIC;
56            rotation_a    : inout STD_LOGIC;
57            rotation_b    : inout STD_LOGIC
58      );
59  end COMPONENT;
60
61      COMPONENT set

```



```
TOP.vhd                                     Wed Jun 18 14:33:08 2008
62     PORT ( rotation_a : in STD_LOGIC;
63           rotation_b : in STD_LOGIC;
64           clk         : in STD_LOGIC;
65           reset       : in STD_LOGIC;
66           out_led     : out STD_LOGIC_VECTOR (6 downto 0);
67           set_led     : inout STD_LOGIC_VECTOR (6 downto 0)
68         );
69     end COMPONENT;
70
71     COMPONENT set_help
72     PORT ( help       : inout STD_LOGIC;
73           start_button : in STD_LOGIC
74         );
75     end COMPONENT;
76     begin
77     Inst_set_help: set_help PORT MAP
78     ( start_button => button_send,
79       help        => help
80     );
81
82
83     Inst_divider: divider PORT MAP
84     (
85       ext_clk_50MHz => clk_system,
86       test          => led_clk_control,
87       dev_clock_out => intern_clk
88     );
89
90     Inst_mac: mac PORT MAP
91     (
92       dat_send      => RS232_DCE_RXD,
93       mac_clk_in    => intern_clk,
94       start_button  => button_send,
95       set_help      => help,
96       dat_send_binaer => dat_send_binaer
97     );
98
99     Inst_rotary_contact_filter: rotary_contact_filter PORT MAP
100    (
101      rotation_a_in => rot_a_in,
102      rotation_b_in => rot_b_in,
103      dev_clk_in   => intern_clk,
104      rotation_a   => rot_a,
105      rotation_b   => rot_b
106    );
107
108     Inst_set: set PORT MAP
109     (
110       rotation_a => rot_a,
111       rotation_b => rot_b,
112       clk        => intern_clk,
113       out_led    => out_led,
114       reset      => reset,
115       set_led    => dat_send_binaer
116     );
117
118     end Behavioral;
```



```

MAC.vhd                                     Wed Jun 18 14:33:17 2008
1  -----
2  --Projekt: Senden mehrerer Zeichen
3  --Instanz: Mac
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity MAC is
13      PORT(
14          dat_send          : out STD_LOGIC;
15          start_button     : in  STD_LOGIC;
16          dat_send_binaer  : in  STD_LOGIC_VECTOR (6 downto 0);
17          mac_clk_in       : in  STD_LOGIC;
18          set_help         : inout STD_LOGIC
19      );
20  end MAC;
21
22  architecture Behavioral of MAC is
23
24  signal counter_index      : integer ;
25  signal help               : STD_LOGIC;
26  signal dat_send_complete  : STD_LOGIC_VECTOR (9 downto 0);
27
28  begin
29  process (mac_clk_in)
30  begin
31  if rising_edge (mac_clk_in) then
32
33      dat_send_complete(9) <= '1';
34      dat_send_complete(8) <= '1';
35      dat_send_complete(7) <= dat_send_binaer(6);
36      dat_send_complete(6) <= dat_send_binaer(5);
37      dat_send_complete(5) <= dat_send_binaer(4);
38      dat_send_complete(4) <= dat_send_binaer(3);
39      dat_send_complete(3) <= dat_send_binaer(2);
40      dat_send_complete(2) <= dat_send_binaer(1);
41      dat_send_complete(1) <= dat_send_binaer(0);
42      dat_send_complete(0) <= '0';
43  end if;
44  end process;
45
46  process (mac_clk_in, start_button)
47  begin
48
49  if rising_edge (mac_clk_in) THEN
50  if (start_button = '1') AND (counter_index < 10) THEN
51  help <= set_help;
52  if help = '0' then
53  if counter_index < 10 THEN
54  counter_index <= counter_index + 1;
55  dat_send <= dat_send_complete(counter_index);
56  else counter_index <= 0;
57  help <= '1';
58  end if;
59  end if;
60  elsif (start_button = '0') AND (counter_index = 10) THEN
61  counter_index <= 0;

```



```
MAC.vhd Wed Jun 18 14:33:17 2008  
62     help <= '1';  
63     elsif start_button = '0' THEN  
64         if help = '0' Then  
65             if counter_index > 0 THEN  
66                 if Counter_index < 10 THEN  
67                     counter_index <= counter_index + 1;  
68                     dat_send <= dat_send_complete(counter_index);  
69                 else Counter_index <= 0;  
70                     help <= '1';  
71                 end if;  
72             end if;  
73         end if;  
74     end if;  
75 end if;  
76 end process;  
77  
78  
79  
80 end Behavioral;  
81
```



```
rotary_contact_filter.vhd                                     Wed Jun 18 14:33:25 2008
1  -----
2  --Projekt: Senden mehrerer Zeichen
3  --Instanz: Rotary-Contact-Filter
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity rotary_contact_filter is
13  Port (      rotation_a_in  : in    STD_LOGIC;
14           rotation_b_in  : in    STD_LOGIC;
15           dev_clk_in     : in    STD_LOGIC;
16           rotation_a     : inout  STD_LOGIC;
17           rotation_b     : inout  STD_LOGIC
18  );
19  end rotary_contact_filter;
20
21  architecture Behavioral of rotary_contact_filter is
22  signal rotation_in : STD_LOGIC_VECTOR (1 downto 0);
23  begin
24  process(dev_clk_in)
25  begin
26      if (rising_edge (dev_clk_in)) then
27          rotation_in <= rotation_b_in & rotation_a_in;
28          case rotation_in is
29              when "00" => rotation_a <= '0';
30                          rotation_b <= rotation_b;
31              when "01" => rotation_a <= rotation_a;
32                          rotation_b <= '0';
33              when "10" => rotation_a <= rotation_a;
34                          rotation_b <= '1';
35              when "11" => rotation_a <= '1';
36                          rotation_b <= rotation_b;
37              when others => rotation_a <= rotation_a;
38                          rotation_b <= rotation_b;
39          end case;
40      end if;
41  end process;
42  end Behavioral;
```



```
SET_vhd                                     Wed Jun 18 14:33:33 2008
1
2
3      -----
4      --Projekt: Senden mehrerer Zeichen
5      --Instanz: Set
6      -----
7
8      library IEEE;
9      use IEEE.STD_LOGIC_1164.ALL;
10     use IEEE.STD_LOGIC_ARITH.ALL;
11     use IEEE.STD_LOGIC_UNSIGNED.ALL;
12
13     ---DREHGEBER-->LEDS_SETZEN---
14     -----
15
16     entity SET is
17     PORT ( rotation_a : in STD_LOGIC;
18           rotation_b : in STD_LOGIC;
19           reset       : in STD_LOGIC;
20           out_led     : out STD_LOGIC_VECTOR (6 downto 0);
21           clk         : in STD_LOGIC;
22           set_led     : inout STD_LOGIC_VECTOR (6 downto 0)
23           );
24
25     end SET;
26
27     architecture Behavioral of SET is
28     begin
29
30     process (reset, rotation_a, rotation_b)
31     begin
32     if reset='1' then
33     set_led <= "0000000";
34     elsif rising_edge(rotation_a) then
35     if rotation_b = '1' then
36     set_led <= set_led - 1;
37     else set_led <= set_led + 1;
38     end if;
39     end if;
40     end process;
41
42     process (clk)
43     begin
44     if rising_edge(clk) then
45     out_led(6) <= set_led(6);
46     out_led(5) <= set_led(5);
47     out_led(4) <= set_led(4);
48     out_led(3) <= set_led(3);
49     out_led(2) <= set_led(2);
50     out_led(1) <= set_led(1);
51     out_led(0) <= set_led(0);
52     end if;
53     end process;
54     end Behavioral;
55
56
```



```
set_help.vhd                                     Wed Jun 18 14:33:40 2008
1  -----
2  --Projekt: Senden mehrerer Zeichen
3  --Instanz: Set_Help
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity set_help is
13  PORT      ( help      : inout STD_LOGIC;
14             start_button : in STD_LOGIC
15             );
16  end set_help;
17
18  architecture Behavioral of set_help is
19
20  signal count : integer;
21  begin
22
23  process ( start_button)
24  begin
25      if rising_edge (start_Button) THEN
26          help <= '0';
27      end if;
28  end process;
29
30
31  end Behavioral;
32
33
```



```
divider.vhd                                     Wed Jun 18 14:33:48 2008
1  -----
2  --Projekt: Senden mehrerer Zeichen
3  --Instanz: Divider
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity divider is
13  port (
14      ext_clk_50MHz      : in      STD_LOGIC;
15      test               : out     STD_LOGIC;
16      dev_clock_out     : inout   STD_LOGIC
17  );
18  end divider;
19
20
21  architecture Behavioral of divider is
22  signal divide_counter : integer := 0;
23
24  begin
25
26  Process(ext_clk_50MHz)
27  begin
28      if (rising_edge (ext_clk_50MHz)) then
29          if (divide_counter /= 2600) then
30              divide_counter <= divide_counter + 1;
31          else
32              divide_counter <= 0;
33              dev_clock_out <= not (dev_clock_out);
34              test <= dev_clock_out ;
35          end if;
36      end if;
37  end process;
38  end Behavioral;
39
40
```





```
TOP.ucf                                     Wed Jun 18 14:33:56 2008
1      #-----
2      #Projekt: Senden mehrerer Zeichen
3      # User Constraint File
4      #-----
5      INST "Inst_mac/dat_send"              INIT = 1;
6      NET "button_send"                    LOC = "K17" | PULLDOWN;
7      NET "clk_system"                    LOC = "C9" ;
8      NET "led_clk_control"                LOC = "F12" ;
9      NET "out_led<0>"                     LOC = "E12" ;
10     NET "out_led<1>"                     LOC = "E11" ;
11     NET "out_led<2>"                     LOC = "F11" ;
12     NET "out_led<3>"                     LOC = "C11" ;
13     NET "out_led<4>"                     LOC = "D11" ;
14     NET "out_led<5>"                     LOC = "E9" ;
15     NET "out_led<6>"                     LOC = "F9" ;
16     NET "reset"                          LOC = "V16" | PULLDOWN ;
17     NET "rot_a_in"                       LOC = "K18" | PULLUP ;
18     NET "rot_b_in"                       LOC = "G18" | PULLUP ;
19     NET "RS232_DCE_RXD"                  LOC = "M14" ;
20
21
```



## A.8 Konstante empfangen

```

TOP.vhd                                     Wed Jun 18 14:12:06 2008
1  -----
2  -- Projekt: Konstante empfangen
3  -- Instanz: Top
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10 entity TOP is
11     PORT (
12         signal_in      : in STD_LOGIC;
13         led_out        : out STD_LOGIC_VECTOR (8 downto 0);
14         test           : out STD_LOGIC;
15         clk_system     : in STD_LOGIC
16     );
17 end TOP;
18
19 architecture Behavioral of TOP is
20
21     signal sample_clk : STD_LOGIC;
22     signal clk_intern : STD_LOGIC;
23
24     COMPONENT MAC
25     PORT (
26         signal_in      : in STD_LOGIC;
27         led_out        : out STD_LOGIC_VECTOR (8 downto 0);
28         sample_clk     : in STD_LOGIC
29     );
30 end COMPONENT;
31
32     COMPONENT divider
33     Port (
34         ext_clk_50MHz : in  STD_LOGIC;
35         test          : out STD_LOGIC;
36         dev_clock_out : inout STD_LOGIC
37     );
38 end COMPONENT;
39
40 begin
41
42     Inst_divider: divider PORT MAP
43     (
44         ext_clk_50MHz => clk_system,
45         test          => test,
46         dev_clock_out => clk_intern
47     );
48
49     Inst_mac: mac PORT MAP
50     (
51         signal_in      => signal_in,
52         led_out        => led_out,
53         sample_clk     => clk_intern
54     );
55
56
57
58
59 end Behavioral;
60
61

```



```
MAC.vhd                                     Wed Jun 18 14:12:20 2008
1
2 -----
3 -- Projekt: Konstante empfangen
4 -- Instanz: Top
5 -----
6
7 library IEEE;
8 use IEEE.STD_LOGIC_1164.ALL;
9 use IEEE.STD_LOGIC_ARITH.ALL;
10 use IEEE.STD_LOGIC_UNSIGNED.ALL;
11
12 entity MAC is
13     PORT
14         signal_in      : in STD_LOGIC;
15         led_out        : out STD_LOGIC_VECTOR (8 downto 0);
16         sample_clk     : in STD_LOGIC
17     );
18 end MAC;
19
20
21 architecture Behavioral of MAC is
22     signal wert        : integer ;
23     signal count       : integer;
24     signal count_led   : integer;
25     signal help        : integer ;
26     signal ausgabe     : STD_LOGIC ;
27
28 begin
29     process (sample_clk)
30     begin
31         if rising_edge (sample_clk) then
32             if signal_in = '0' then
33                 help <= 1;
34                 wert <= 0;
35             end if;
36             if help = 1 then
37                 count <= count + 1;
38                 if signal_in = '1' then
39                     wert <= wert + 1;
40                 end if;
41                 if count = 15 then -- 1 Bit empfangen
42                     count_led <= count_led + 1;
43                     if wert > 8 then -- Empf. Bit =1
44                         ausgabe <= '1';
45                         wert <= 0;
46                     else -- Empf. Bit =0
47                         ausgabe <= '0';
48                         wert <= 0;
49                     end if;
50                     led_out(count_led) <= ausgabe;
51                     count <= 0 ;
52                     if count_led = 9 then
53                         count_led <= 0;
54                         help <= 0;
55                         wert <= 0;
56                     end if;
57                 end if;
58             end if;
59         end if;
60     end process;
61 end Behavioral;
```



```
DIVIDER.vhd                                     Wed Jun 18 14:12:27 2008
1  -----
2  -- Projekt: Konstante empfangen
3  -- Instanz: Top
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10 entity divider is
11     Port (
12         ext_clk_50MHz : in     STD_LOGIC;
13         test          : out    STD_LOGIC;
14         dev_clock_out : inout  STD_LOGIC
15     );
16 end divider;
17
18
19 architecture Behavioral of divider is
20     signal divide_counter : integer := 0;
21
22
23 begin
24
25     Process(ext_clk_50MHz)
26     begin
27         if (rising_edge (ext_clk_50MHz)) then
28             if (divide_counter /= 2600) then
29                 divide_counter <= divide_counter + 1;
30             else
31                 divide_counter <= 0;
32                 dev_clock_out <= not ( dev_clock_out);
33                 test <= dev_clock_out ;
34             end if;
35         end if;
36     end process;
37 end Behavioral;
38
39
40
```



```
TOP.ucf                                     Wed Jun 18 14:12:34 2008
1      #-----
2      #Projekt: Konstante empfangen
3      # User Constraint File
4      #-----
5      NET "clk_system" LOC = "C9" ;
6      NET "led_out<2>" LOC = "F12" ;
7      NET "led_out<3>" LOC = "E12" ;
8      NET "led_out<4>" LOC = "E11" ;
9      NET "led_out<5>" LOC = "F11" ;
10     NET "led_out<6>" LOC = "C11" ;
11     NET "led_out<7>" LOC = "D11" ;
12     NET "led_out<8>" LOC = "E9" ;
13     NET "signal_in" LOC = "R7" ;
```



## A.9 Senden und Empfangen

```

top.vhd                                     Wed Jun 18 14:57:43 2008
1
2  -----
3  --Projekt: Senden und Empfangen
4  --Instanz: Top
5  -----
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12  entity top is
13      PORT (
14          clk_system      : in   STD_LOGIC;
15          rot_a_in        : in   STD_LOGIC;
16          signal_in       : in   STD_LOGIC;
17          rot_b_in        : in   STD_LOGIC;
18          reset           : in   STD_LOGIC;
19          button_send     : in   STD_LOGIC;
20          set_led         : inout STD_LOGIC_VECTOR (7 downto 0);
21          led_out         : out  STD_LOGIC_VECTOR (9 downto 0);
22          RS232_DCE_RXD   : out  STD_LOGIC;
23          out_led_sig     : out  STD_LOGIC_VECTOR (7 downto 0)
24      );
25  end top;
26
27  architecture Behavioral of top is
28
29      signal rot_a          : STD_LOGIC;
30      signal rot_b          : STD_LOGIC;
31      signal dat_send_binaer : STD_LOGIC_VECTOR (7 downto 0);
32      signal intern_clk     : STD_LOGIC;
33      signal test           : STD_LOGIC;
34      signal led_clk_control : STD_LOGIC;
35      signal help           : STD_LOGIC;
36      signal edge_detect_sig : STD_LOGIC;
37      signal clk16         : STD_LOGIC;
38
39      COMPONENT MAC_receive is
40          PORT
41              (
42                  signal_in      : in  STD_LOGIC;
43                  led_out        : out STD_LOGIC_VECTOR (9 downto 0);
44
45                  sample_clk     : in  STD_LOGIC
46              );
47      end COMPONENT;
48
49      COMPONENT set_help is
50          PORT
51              (
52                  help           : inout STD_LOGIC;
53                  start_button : in   STD_LOGIC
54              );
55      end COMPONENT;
56
57      COMPONENT MAC is
58          PORT(
59              dat_send      : out  STD_LOGIC;
60              start_button  : in   STD_LOGIC;
61              set_help      : inout STD_LOGIC;
62              dat_send_binaer : in  STD_LOGIC_VECTOR (7 downto 0);
63              mac_clk_in    : in   STD_LOGIC
64          );

```



```
top.vhd                                     Wed Jun 18 14:57:44 2008
61     );
62 end COMPONENT;
63
64 COMPONENT SET is
65     PORT (      rotation_a : in  STD_LOGIC;
66                rotation_b : in  STD_LOGIC;
67                reset       : in  STD_LOGIC;
68                out_led     : out STD_LOGIC_VECTOR (7 downto 0);
69                clk         : in  STD_LOGIC;
70                set_led     : inout STD_LOGIC_VECTOR (7 downto 0)
71            );
72
73 end COMPONENT;
74
75
76
77 COMPONENT rotary_contact_filter is
78     Port ( rotation_a_in  : in   STD_LOGIC;
79            rotation_b_in : in   STD_LOGIC;
80            dev_clk_in    : in   STD_LOGIC;
81            rotation_a    : inout STD_LOGIC;
82            rotation_b    : inout STD_LOGIC
83        );
84 end COMPONENT;
85
86 COMPONENT divider is
87     Port (      ext_clk_50MHz : in   STD_LOGIC;
88                test          : out  STD_LOGIC;
89                dev_clock_out : inout STD_LOGIC
90            );
91 end COMPONENT;
92
93
94
95 COMPONENT divider16 is
96     Port (      ext_clk_50MHz : in   STD_LOGIC;
97                test          : out  STD_LOGIC;
98                dev_clock_out : inout STD_LOGIC
99            );
100 end COMPONENT;
101
102
103
104 begin
105
106
107
108
109 Inst_set_help: set_help PORT MAP
110     ( help      => help,
111       start_button => button_send
112     );
113
114
115 Inst_divider: divider PORT MAP
116     (
117       ext_clk_50MHz => clk_system,
118       test          => led_clk_control,
119       dev_clock_out => intern_clk
120     );
121
```



```
top.vhd                                     Wed Jun 18 14:57:44 2008
122   Inst_mac: mac PORT MAP
123   (
124       dat_send      => RS232_DCE_RXD,
125       mac_clk_in   => intern_clk,
126       start_button => button_send,
127       set_help     => help,
128       dat_send_binaer => dat_send_binaer
129   );
130
131   Inst_rotary_contact_filter: rotary_contact_filter PORT MAP
132   (
133       rotation_a_in => rot_a_in,
134       rotation_b_in => rot_b_in,
135       dev_clk_in   => intern_clk,
136       rotation_a   => rot_a,
137       rotation_b   => rot_b
138   );
139
140   Inst_set: set PORT MAP
141   (
142       rotation_a   => rot_a,
143       rotation_b   => rot_b,
144       clk          => intern_clk,
145       out_led      => out_led_sig,
146       reset        => reset,
147       set_led      => dat_send_binaer
148   );
149
150   Inst_mac_receive: mac_receive PORT MAP
151   (
152       signal_in    => signal_in,
153       led_out      => led_out,
154       sample_clk   => clk16
155   );
156
157
158
159   INST_divider16: divider16 PORT MAP
160   (
161       ext_clk_50MHz => clk_system,
162       test          => test,
163       dev_clock_out => clk16
164   );
165
166
167   end Behavioral;
168
169
170
```





```
MAC_vhd                                     Wed Jun 18 14:57:50 2008
1  -----
2  --Projekt: Senden und Empfangen
3  --Instanz: Mac-Receive
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity MAC_receive is
13  port
14      signal_in      : in STD_LOGIC;
15      led_out        : out STD_LOGIC_VECTOR (9 downto 0);
16      sample_clk     : in STD_LOGIC
17  );
18  end MAC_receive;
19
20  architecture Behavioral of MAC_receive is
21
22  signal help : integer ;
23
24  begin
25  process (sample_clk)
26
27  variable count_led : integer;
28  variable wert      : integer ;
29  variable count     : integer;
30  variable vergleich : STD_LOGIC_VECTOR (1 downto 0);
31  variable edge      : STD_LOGIC ;
32  variable ausgabe   : STD_LOGIC ;
33  begin
34
35  if rising_edge (sample_clk) then
36  vergleich := vergleich(0)& signal_in;
37  case vergleich is
38  when "00" => edge := '0';
39  when "01" => edge := '1';
40  when "10" => edge := '1';
41  when "11" => edge := '0';
42  when others => vergleich := vergleich;
43  end case;
44
45  if signal_in = '0' then
46  help <= 1;
47  wert := 0;
48  end if;
49  if help = 1 then
50  count := count + 1;
51  if signal_in = '1' then
52  wert := wert + 1;
53  end if;
54  if count = 15 then
55  count_led := count_led + 1;
56  if wert > 8 then
57  ausgabe := '1';
58  wert := 0;
59  else
60  ausgabe := '0';
61  wert := 0;
62  end if;
63  end if;
64  end if;
65  end if;
66  end process;
67  end Behavioral;
68  end MAC_receive;
```



```
MAC.vhd Wed Jun 18 14:57:50 2008  
62         if edge = '1' then  
63             count := 0;  
64         end if;  
65         led_out(count_led) <= ausgabe;  
66         count := 0 ;  
67         if count_led = 10 then  
68             count_led := 0;  
69             help <= 0;  
70             wert := 0;  
71         end if;  
72     end if;  
73 end if;  
74 end if;  
75 end process;  
76 end Behavioral;
```



```

MAC_send.vhd                                     Wed Jun 18 14:57:59 2008
1  -----
2  --Projekt: Senden und Empfangen
3  --Instanz: Mac [send]
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity MAC is
13  PORT(
14      dat_send          : out  STD_LOGIC;
15      start_button     : in   STD_LOGIC;
16      dat_send_binaer  : in   STD_LOGIC_VECTOR (7 downto 0);
17      mac_clk_in       : in   STD_LOGIC;
18      set_help         : inout STD_LOGIC
19  );
20  end MAC;
21
22  architecture Behavioral of MAC is
23
24  signal counter_index      : integer ;
25  signal help              : STD_LOGIC;
26  signal dat_send_complete : STD_LOGIC_VECTOR (9 downto 0);
27
28  begin
29  process (mac_clk_in)
30  begin
31  if rising_edge (mac_clk_in) then
32
33      dat_send_complete(9) <= '1';
34      dat_send_complete(8) <= dat_send_binaer(7);
35      dat_send_complete(7) <= dat_send_binaer(6);
36      dat_send_complete(6) <= dat_send_binaer(5);
37      dat_send_complete(5) <= dat_send_binaer(4);
38      dat_send_complete(4) <= dat_send_binaer(3);
39      dat_send_complete(3) <= dat_send_binaer(2);
40      dat_send_complete(2) <= dat_send_binaer(1);
41      dat_send_complete(1) <= dat_send_binaer(0);
42      dat_send_complete(0) <= '0';
43  end if;
44  end process;
45
46  process (mac_clk_in, start_button)
47  begin
48
49  if rising_edge (mac_clk_in) THEN
50  if (start_button = '1') AND (counter_index < 10) THEN
51  help <= set_help;
52  if help = '0' then
53  if counter_index < 10 THEN
54  counter_index <= counter_index + 1;
55  dat_send <= dat_send_complete(counter_index);
56  else counter_index <= 0;
57  help <= '1';
58  end if;
59  end if;
60  elsif (start_button = '0') AND (counter_index = 10) THEN
61  counter_index <= 0;

```



```
MAC_send.vhd                                     Wed Jun 18 14:57:59 2008
62      help <= '1';
63      elsif start_button = '0' THEN
64          if help = '0' Then
65              if counter_index > 0 THEN
66                  if Counter_index < 10 THEN
67                      counter_index <= counter_index + 1;
68                      dat_send <= dat_send_complete(counter_index);
69                  else Counter_index <= 0;
70                      help <= '1';
71                  end if;
72              end if;
73          end if;
74      end if;
75  end if;
76  end process;
77
78
79
80  end Behavioral;
81
```



```
Filter.vhd                                     Wed Jun 18 14:58:06 2008
1  -----
2  --Projekt: Senden und Empfangen
3  --Instanz: Rotary_Contact_Filter
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity rotary_contact_filter is
13  port ( rotation_a_in   : in   STD_LOGIC;
14        rotation_b_in   : in   STD_LOGIC;
15        dev_clk_in      : in   STD_LOGIC;
16        rotation_a      : inout STD_LOGIC;
17        rotation_b      : inout STD_LOGIC
18  );
19  end rotary_contact_filter;
20
21  architecture Behavioral of rotary_contact_filter is
22  signal rotation_in : STD_LOGIC_VECTOR (1 downto 0);
23  begin
24  process(dev_clk_in)
25  begin
26  if (rising_edge (dev_clk_in)) then
27  rotation_in <= rotation_b_in & rotation_a_in;
28  case rotation_in is
29  when "00" => rotation_a <= '0';
30  rotation_b <= rotation_b;
31  when "01" => rotation_a <= rotation_a;
32  rotation_b <= '0';
33  when "10" => rotation_a <= rotation_a;
34  rotation_b <= '1';
35  when "11" => rotation_a <= '1';
36  rotation_b <= rotation_b;
37  when others => rotation_a <= rotation_a;
38  rotation_b <= rotation_b;
39  end case;
40  end if;
41  end process;
42  end Behavioral;
43
44
45
```



```
set.vhd                                     Wed Jun 18 14:58:12 2008
1  -----
2  --Projekt: Senden und Empfangen
3  --Instanz: Set
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity SET is
13      PORT ( rotation_a   : in   STD_LOGIC;
14            rotation_b   : in   STD_LOGIC;
15            reset        : in   STD_LOGIC;
16            out_led      : out  STD_LOGIC_VECTOR (7 downto 0);
17            clk          : in   STD_LOGIC;
18            set_led      : inout STD_LOGIC_VECTOR (7 downto 0)
19            );
20
21  end SET;
22
23  architecture Behavioral of SET is
24  begin
25
26  process (reset, rotation_a, rotation_b)
27  begin
28  if reset='1' then
29  set_led <= "00000000";
30  elsif rising_edge (rotation_a) then
31  if rotation_b = '1' then
32  set_led <= set_led -1;
33  else set_led <= set_led +1;
34  end if;
35  end if;
36  end process;
37
38  process (clk)
39  begin
40  if rising_edge (clk) then
41  out_led(7) <= set_led(7);
42  out_led(6) <= set_led(6);
43  out_led(5) <= set_led(5);
44  out_led(4) <= set_led(4);
45  out_led(3) <= set_led(3);
46  out_led(2) <= set_led(2);
47  out_led(1) <= set_led(1);
48  out_led(0) <= set_led(0);
49  end if;
50
51  end process;
52  end Behavioral;
53
54
55
56
57
58
```



```
set_help.vhd                                     Wed Jun 18 14:58:20 2008
1  -----
2  --Projekt: Senden und Empfangen
3  --Instanz: Set_Help
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity set_help is
13  PORT ( help          : inout STD_LOGIC;
14         start_button : in  STD_LOGIC
15        );
16  end set_help;
17
18  architecture Behavioral of set_help is
19
20  begin
21
22  process ( start_button)
23  begin
24      if rising_edge (start_Button) THEN
25          help <= '0';
26      end if;
27  end process;
28
29
30  end Behavioral;
31
32
```



```
DIVIDER16.vhd                                     Wed Jun 18 14:58:27 2008
1  -----
2  --Projekt: Senden und Empfangen
3  --Instanz: Divider16
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10 entity divider16 is
11     Port (
12         ext_clk_50MHz    : in  STD_LOGIC;
13         test             : out STD_LOGIC;
14         dev_clock_out    : inout STD_LOGIC
15     );
16 end divider16;
17
18 architecture Behavioral of divider16 is
19     signal divide_counter : integer := 0;
20
21 begin
22
23     Process(ext_clk_50MHz)
24     begin
25         if (rising_edge (ext_clk_50MHz)) then
26             if (divide_counter /= 162) then
27                 divide_counter <= divide_counter + 1;
28             else
29                 divide_counter <= 0;
30                 dev_clock_out <= not ( dev_clock_out);
31                 test <= dev_clock_out ;
32             end if;
33         end process;
34     end Behavioral;
35
36
37
38
39
```





```
DIVIDER.vhd Wed Jun 18 14:58:34 2008
1 -----
2 --Projekt: Senden und Empfangen
3 --Instanz: Divider
4 -----
5 library IEEE;
6 use IEEE.STD_LOGIC_1164.ALL;
7 use IEEE.STD_LOGIC_ARITH.ALL;
8 use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10 entity divider is
11     Port (
12         ext_clk_50MHz : in    STD_LOGIC;
13         test          : out   STD_LOGIC;
14         dev_clock_out : inout STD_LOGIC
15     );
16 end divider;
17
18 architecture Behavioral of divider is
19     signal divide_counter : integer := 0;
20
21 begin
22
23     Process(ext_clk_50MHz)
24     begin
25         if (rising_edge(ext_clk_50MHz)) then
26             if (divide_counter /= 2600) then
27                 divide_counter <= divide_counter + 1;
28             else
29                 divide_counter <= 0;
30                 dev_clock_out <= not (dev_clock_out);
31                 test <= dev_clock_out ;
32             end if;
33         end process;
34     end Behavioral;
35
36
37
38
39
40
```



```
top.ucf                                     Wed Jun 18 14:58:40 2008
1  #-----
2  #Projekt: Senden und Empfangen
3  # User Constraint File
4  #-----
5  NET "led_out<9>" LOC = "F9" ;
6  NET "led_out<8>" LOC = "E9" ;
7  NET "led_out<7>" LOC = "D11" ;
8  NET "led_out<6>" LOC = "C11" ; # LED - PC -> Board
9  NET "led_out<5>" LOC = "F11" ;
10 NET "led_out<4>" LOC = "E11" ;
11 NET "led_out<3>" LOC = "E12" ;
12 NET "led_out<2>" LOC = "F12" ;
13 #-----
14 #NET "out_led_sig<0>" LOC = "F9" ;
15 #NET "out_led_sig<1>" LOC = "E9" ;
16 #NET "out_led_sig<2>" LOC = "D11" ;
17 #NET "out_led_sig<3>" LOC = "C11" ; #LED Board -> PC
18 #NET "out_led_sig<4>" LOC = "F11" ;
19 #NET "out_led_sig<5>" LOC = "E11" ;
20 #NET "out_led_sig<6>" LOC = "E12" ;
21
22
23 INST "Inst_mac/dat_send" INIT = 1;
24 NET "button_send" LOC = "K17" | PULLDOWN ;
25 NET "clk_system" LOC = "C9" ;
26 NET "reset" LOC = "V16" | PULLDOWN;
27 NET "rot_a_in" LOC = "K18" | PULLUP ;
28 NET "rot_b_in" LOC = "G18" | PULLUP ;
29 NET "RS232_DCE_RXD" LOC = "M14" ;
30 NET "signal_in" LOC = "R7" ;
31
32
33
```



## A.10 LC - Display

```

top.vhd                                     Wed Jun 25 11:58:31 2008
1
2  -----
3  --Projekt: LC Display
4  --Instanz: Top
5  -----
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11  entity top is
12  PORT ( clock_50MHz      : in   STD_LOGIC;
13         lcd_dat         : inout STD_LOGIC_VECTOR (3 downto 0);
14         lcd_e           : out   STD_LOGIC;
15         lcd_rw          : out   STD_LOGIC;
16         lcd_rs          : out   STD_LOGIC
17       );
18  end top;
19
20  architecture Behavioral of top is
21
22  signal intern_clk      : STD_LOGIC;
23  signal count           : STD_LOGIC_VECTOR (10 downto 0);
24
25  Component divider is
26  Port (
27      ext_clk_50MHz      : in   STD_LOGIC;
28      dev_clock_out     : inout STD_LOGIC
29  );
30  end Component;
31
32  Component mac is
33  PORT ( clock           : in   STD_LOGIC;
34         lcd_dat        : inout STD_LOGIC_VECTOR (3 downto 0);
35         lcd_e          : out   STD_LOGIC;
36         lcd_rw         : out   STD_LOGIC;
37         count          : in   STD_LOGIC_VECTOR (10 downto 0);
38         lcd_rs         : out   STD_LOGIC
39       );
40  end Component;
41
42  COMPONENT counter is
43  PORT (
44      clock : in   STD_LOGIC;
45      count : inout STD_LOGIC_VECTOR (10 downto 0)
46  );
47  end COMPONENT;
48  begin
49
50  Inst_counter: counter PORT MAP
51  (
52      clock => intern_clk,
53      count => count
54  );
55
56  Inst_mac: mac PORT MAP
57  (
58      clock      => intern_clk,
59      lcd_dat    => lcd_dat,
60      lcd_e      => lcd_e,
61      lcd_rw     => lcd_rw,

```



```
top.vhd                                     Wed Jun 25 11:58:31 2008
62         lcd_rs      => lcd_rs,
63         count       => count
64     );
65
66     Inst_divider: divider PORT MAP
67     (
68         ext_clk_50MHz => Clock_50MHZ,
69         dev_clock_out => intern_clk
70     );
71
72     end Behavioral;
73
74
75
76
77
78
79
80
81
82
83
84
85
86
```



```

mac.vhd                                     Wed Jun 25 11:58:43 2008
1
2 -----
3 --Projekt: LC Display
4 --Instanz: Mac
5 -----
6 library IEEE;
7 use IEEE.STD_LOGIC_1164.ALL;
8 use IEEE.STD_LOGIC_ARITH.ALL;
9 use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12 entity mac is
13 PORT ( clock      : in   STD_LOGIC;
14       lcd_dat     : out  STD_LOGIC_VECTOR (3 downto 0);
15       lcd_e       : out  STD_LOGIC;
16       lcd_rw      : out  STD_LOGIC;
17       count       : in   STD_LOGIC_VECTOR (10 downto 0);
18       lcd_rs      : out  STD_LOGIC
19 );
20 end mac;
21
22 architecture Behavioral of mac is
23 begin
24
25 process (clock)
26 variable onecycle: STD_LOGIC := '0';
27 begin
28 if rising_edge (clock) then
29 if onecycle = '0' Then
30 case count is
31 when "01011101110" => lcd_dat <= "0011";  ----750
32                      lcd_e  <= '0';
33                      lcd_rs <= '0';
34                      lcd_rw <= '0';
35 when "01011101111" => lcd_e  <= '1';  ----751
36 when "01110111101" => lcd_e  <= '1';  ----957
37 when "01111000011" => lcd_e  <= '1';  ----963
38 when "01111000110" => lcd_dat <= "0010"; ----966
39 when "01111000111" => lcd_e  <= '1';  ----967
40 when "01111001010" => lcd_dat <= "0001";
41 when "01111001011" => lcd_e  <= '1';
42 when "01111001110" => lcd_dat <= "1100";  --- function set
43 when "01111001111" => lcd_e  <= '1';  -----
44 when "01111010001" => lcd_dat <= "0000";
45 when "01111010010" => lcd_e  <= '1';  ----- entry mode
46 when "01111010100" => lcd_dat <= "0110";
47 when "01111010101" => lcd_e  <= '1';  -----
48 when "01111010110" => lcd_dat <= "0000";
49 when "01111010111" => lcd_e  <= '1';  ----- display control
50 when "01111011001" => lcd_dat <= "1100";
51 when "01111011010" => lcd_e  <= '1';  -----
52 when "01111011100" => lcd_dat <= "0000";
53 when "01111011101" => lcd_e  <= '1';  --- display clear
54 when "01111011111" => lcd_dat <= "0001";
55 when "01111100000" => lcd_e  <= '1';  -----
56 when "11000000000" => lcd_dat <= "0000";
57 when "11000000010" => lcd_e  <= '1';
58 when "11000000100" => lcd_dat <= "1101";
59 when "11000000101" => lcd_e  <= '1';  -----
60 when "11000001000" => lcd_dat <= "0100";
61                      lcd_rs <= '1';

```



```

mac_vhd                                     Wed Jun 25 11:58:43 2008
62     when "11000001010" => lcd_e  <= '1';
63     when "11000001100" => lcd_dat <= "1000";
64     when "11000010000" => lcd_e  <= '1';          ----- H
65     -----
66     when "11000011000" => lcd_dat <= "0100";
67     when "11000011011" => lcd_e  <= '1';
68     when "11000011110" => lcd_dat <= "0101";
69     when "11000100010" => lcd_e  <= '1';          ----- E
70     -----
71     when "11000101000" => lcd_dat <= "0100";
72     when "11000101011" => lcd_e  <= '1';
73     when "11000101111" => lcd_dat <= "1100";
74     when "11000110010" => lcd_e  <= '1';          ----- L
75     -----
76     when "11000110100" => lcd_dat <= "0100";
77     when "11000111000" => lcd_e  <= '1';
78     when "11000111010" => lcd_dat <= "1100";
79     when "11000111100" => lcd_e  <= '1';          ----- L
80     -----
81     when "11000111110" => lcd_dat <= "0100";
82     when "11001000001" => lcd_e  <= '1';
83     when "11001000100" => lcd_dat <= "1111";
84     when "11001000111" => lcd_e  <= '1';          ----- O
85     -----
86     when "11001001001" => lcd_dat <= "0010";
87     when "11001001011" => lcd_e  <= '1';
88     when "11001001101" => lcd_dat <= "0000";
89     when "11001001111" => lcd_e  <= '1';          -----
90     -----
91     when "11001010001" => lcd_dat <= "0101";
92     when "11001010011" => lcd_e  <= '1';
93     when "11001010101" => lcd_dat <= "0111";
94     when "11001010111" => lcd_e  <= '1';          ----- W
95     -----
96     when "11001011001" => lcd_dat <= "0100";
97     when "11001011011" => lcd_e  <= '1';
98     when "11001011101" => lcd_dat <= "1111";
99     when "11001011111" => lcd_e  <= '1';          ----- O
100    -----
101    when "11001100011" => lcd_dat <= "0101";
102    when "11001100110" => lcd_e  <= '1';
103    when "11001101001" => lcd_dat <= "0010";
104    when "11001101011" => lcd_e  <= '1';          ----- R
105    -----
106    when "11001110000" => lcd_dat <= "0100";
107    when "11001110010" => lcd_e  <= '1';
108    when "11001110100" => lcd_dat <= "1100";
109    when "11001110111" => lcd_e  <= '1';          ----- L
110    -----
111    when "11010000000" => lcd_dat <= "0100";
112    when "11010000011" => lcd_e  <= '1';
113    when "11010000101" => lcd_dat <= "0100";
114    when "11010001000" => lcd_e  <= '1';          ----- D
115    -----
116    when "11111111111" => onecycle := '1';
117    when others          => lcd_e  <= '0';
118  end case;
119  end if;
120  end if;
121  end process;
122  end Behavioral;

```



```
counter.vhd                                     Wed Jun 25 11:58:53 2008
1  -----
2  --Projekt: LC Display
3  --Instanz: Counter
4  -----
5  use IEEE.STD_LOGIC_1164.ALL;
6  use IEEE.STD_LOGIC_ARITH.ALL;
7  use IEEE.STD_LOGIC_UNSIGNED.ALL;
8
9
10 entity counter is
11     PORT (
12         clock : in  STD_LOGIC;
13         count  : inout STD_LOGIC_VECTOR (10 downto 0)
14     );
15 end counter;
16
17 architecture Behavioral of counter is
18
19 begin
20 process (clock)
21 begin
22     if rising_edge (clock) THEN
23         count <= count + '1';
24     end if;
25 end process;
26 end Behavioral;
27
28
29
30
31
32
33
34
35
36
37
38
```



```
divider.vhd                                     Wed Jun 25 11:59:00 2008
1  -----
2  --Projekt: LC Display
3  --Instanz: Divider
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity divider is
13  port (
14      ext_clk_50MHz      : in    STD_LOGIC;
15      dev_clock_out     : inout  STD_LOGIC --25 kHz
16  );
17  end divider;
18
19
20  architecture Behavioral of divider is
21  signal divide_counter : integer := 0;
22
23
24  begin
25
26  Process(ext_clk_50MHz)
27  begin
28      if (rising_edge (ext_clk_50MHz)) then
29          if (divide_counter /= 1000) then
30              divide_counter <= divide_counter + 1;
31          else
32              divide_counter <= 0;
33              dev_clock_out <= not (dev_clock_out);
34          end if;
35      end if;
36  end process;
37  end Behavioral;
38
```





```
top.ucf                                     Wed Jun 25 11:59:08 2008
1      #-----
2      #Projekt: LC Display
3      #   User Constraint File
4      #-----
5      NET "clock_50MHz" LOC = "C9" ;
6      NET "lcd_dat<0>" LOC = "R15" ;
7      NET "lcd_dat<1>" LOC = "R16" ;
8      NET "lcd_dat<2>" LOC = "P17" ;
9      NET "lcd_dat<3>" LOC = "M15" ;
10     NET "lcd_e" LOC = "M18" ;
11     NET "lcd_rs" LOC = "L18" ;
12     NET "lcd_rw" LOC = "L17" ;
13
14
```



## A.11 Verstärkung einstellen

```

top.vhd                                     Wed Jun 18 16:10:52 2008
1
2  -----
3  --Projekt: Verstärkung einstellen
4  -- Instanz: Top
5  -----
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11  entity top is
12  PORT (
13      clk_system   : in   STD_LOGIC ;
14      start_button : in   STD_LOGIC;
15      sdi          : out  STD_LOGIC;
16      sck_out      : inout STD_LOGIC;
17      amp_cs       : out  STD_LOGIC
18  );
19  end top;
20
21  architecture Behavioral of top is
22
23  signal help          : STD_LOGIC;
24  signal count_set_gain_sig : STD_LOGIC_VECTOR (3 downto 0);
25
26
27  COMPONENT setgain is
28  PORT (
29      amp_cs : out   STD_LOGIC;
30      sck    : in   STD_LOGIC; -- 1 MHz Takt
31      sdi    : out  STD_LOGIC;
32      count  : in   STD_LOGIC_VECTOR (3 downto 0)
33  );
34  end COMPONENT;
35
36  COMPONENT divider is
37  Port (
38      ext_clk_50MHz : in   STD_LOGIC;
39      dev_clock_out : inout STD_LOGIC
40  );
41  end COMPONENT;
42
43  COMPONENT count_set_gain is
44  PORT (
45      clock          : in   STD_LOGIC;
46      start_button   : in   STD_LOGIC;
47      set_help       : in   STD_LOGIC;
48      count_set_gain_i : inout STD_LOGIC_VECTOR( 3 downto 0)
49  );
50  end COMPONENT;
51
52
53  COMPONENT set_help is
54  PORT ( help : inout STD_LOGIC;
55          start_button : in   STD_LOGIC
56  );
57  end COMPONENT;
58
59
60  begin
61

```



```
top.vhdWed Jun 18 16:10:52 2008  
62   Inst_setgain: setgain PORT MAP  
63   (  
64       amp_cs => amp_cs,  
65       sck    => sck_out,  
66       sdi    => sdi,  
67       count  => count_set_gain_sig  
68   );  
69  
70  
71   Inst_divider: divider PORT MAP  
72   ( ext_clk_50MHz => clk_system,  
73     dev_clock_out => sck_out  
74   );  
75  
76   Inst_set_help: set_help PORT MAP  
77   (  
78       help      => help,  
79       start_button => start_button  
80   );  
81  
82   Inst_count_set_gain: count_set_gain PORT MAP  
83   (  
84       clock      => sck_out,  
85       start_button => start_button,  
86       set_help    => help,  
87       count_set_gain_i => count_set_gain_sig  
88   );  
89  
90   end Behavioral;  
91  
92
```



```
setgain.vhd                                     Wed Jun 18 16:10:58 2008
1  -----
2  --Projekt: Verstärkung einstellen
3  -- Instanz: Setgain
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10 entity setgain is
11     PORT (
12         amp_cs : out STD_LOGIC;
13         sck    : in  STD_LOGIC;  -- 1 MHz Takt
14         sdi    : out STD_LOGIC;
15         count  : in  STD_LOGIC_VECTOR (3 downto 0)
16     );
17 end setgain;
18
19 architecture Behavioral of setgain is
20
21     signal gain : STD_LOGIC_VECTOR (7 downto 0) := "00010001" ; -- gain = -1 für Kanal A und
22     -----
23     --gain -1 : 0001
24     --      -2 : 0010
25     --      -5 : 0011
26     --     -10 : 0100
27     --     -20 : 0101
28     --     -50 : 0110
29     --    -100: 0111
30     -----
31 begin
32
33     process (sck)
34     begin
35         if rising_edge (sck) THEN
36             case count is
37                 when "0001" => amp_cs <= '0';
38                 when "0010" => sdi  <= gain(7);
39                 when "0011" => sdi  <= gain(6);
40                 when "0100" => sdi  <= gain(5);
41                 when "0101" => sdi  <= gain(4);
42                 when "0110" => sdi  <= gain(3);
43                 when "0111" => sdi  <= gain(2);
44                 when "1000" => sdi  <= gain(1);
45                 when "1001" => sdi  <= gain(0);
46                 when "1010" => amp_cs <= '1';
47                 when others => amp_cs <= '1';
48             end case;
49         end if;
50     end process;
51 end Behavioral;
52
53
```



```

count_set_gain.vhd                                     Wed Jun 18 16:11:08 2008
1  -----
2  --Projekt: Verstärkung einstellen
3  -- Instanz: Count_set_Gain
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12
13  entity count_set_gain is
14
15      PORT (
16          clock          : in  STD_LOGIC;
17          start_button   : in  STD_LOGIC;
18          set_help       : in  STD_LOGIC;
19          count_set_gain_i : inout STD_LOGIC_VECTOR ( 3 downto 0)
20      );
21
22  end count_set_gain;
23
24  architecture Behavioral of count_set_gain is
25
26      signal Counter_index : integer;
27      signal help          : STD_LOGIC;
28
29  begin
30      process (clock, start_button)
31      begin
32          if rising_edge (clock) THEN
33              if (start_button = '1') AND (counter_index < 11) THEN
34                  help <= set_help;
35                  if help = '0' then
36                      if counter_index < 12 THEN
37                          counter_index <= counter_index + 1;
38                          count_set_gain_i <= count_set_gain_i + '1';
39                          else counter_index <= 0;
40                          help <= '1';
41                      end if;
42                  end if;
43              elsif (start_button = '0') AND (counter_index = 11) THEN
44                  counter_index <= 0;
45                  help <= '1';
46              elsif start_button = '0' THEN
47                  if help = '0' Then
48                      if counter_index > 0 THEN
49                          if Counter_index < 11 THEN
50                              counter_index <= counter_index + 1;
51                              count_set_gain_i <= count_set_gain_i + 1;
52                          else Counter_index <= 0;
53                          help <= '1';
54                      end if;
55                  end if;
56              end if;
57          end if;
58      end process;
59  end Behavioral;
60

```



```
set_help.vhd                                     Wed Jun 18 16:11:16 2008
1  -----
2  --Projekt: Verstärkung einstellen
3  -- Instanz: Set_Help
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity set_help is
13  PORT      ( help          : inout STD_LOGIC;
14             start_button : in   STD_LOGIC
15             );
16  end set_help;
17
18  architecture Behavioral of set_help is
19
20  begin
21
22  process ( start_button)
23  begin
24      if rising_edge (start_Button) THEN
25          help <= '0';
26      end if;
27  end process;
28
29  end Behavioral;
30
31
```



```
divider.vhd                                     Wed Jun 18 16:11:25 2008
1  -----
2  --Projekt: Verstärkung einstellen
3  -- Instanz: Divider
4  -----
5
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12  entity divider is
13  Port (
14      ext_clk_50MHz      : in   STD_LOGIC;
15      dev_clock_out     : inout STD_LOGIC -- 1MHz
16  );
17  end divider;
18
19  architecture Behavioral of divider is
20  signal divide_counter : integer := 0;
21
22  begin
23
24  Process(ext_clk_50MHz)
25  begin
26      if (rising_edge (ext_clk_50MHz)) then
27          if (divide_counter /= 25) then
28              divide_counter <= divide_counter + 1;
29          else
30              divide_counter <= 0;
31              dev_clock_out <= not ( dev_clock_out);
32          end if;
33      end if;
34  end process;
35  end Behavioral;
36
37
```



```
top.ucf                                     Wed Jun 18 16:11:32 2008
1      #-----
2      #Projekt: Verstärkung einstellen
3      #   User Constraint File
4      #-----
5      NET "amp_cs"      LOC = "N7"  ;
6      NET "clk_system" LOC = "C9"  ;
7      NET "sck_out"    LOC = "U16" ;
8      NET "sdi"        LOC = "T4"  ;
9      NET "start_button" LOC = "R17" ;
10
11
```





## A.12 Verstärkung anzeigen

```

top.vhd                                     Wed Jun 18 16:23:08 2008
1
2  -----
3  --Projekt: Verstärkung anzeigen
4  --Instanz: Top
5  -----
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11  entity top is
12  port (
13      clk_system      : in    STD_LOGIC ;
14      start_button    : in    STD_LOGIC;
15      sdi              : out   STD_LOGIC;
16      sck_out         : inout  STD_LOGIC;
17      amp_do          : in    STD_LOGIC;
18      amp_cs          : inout  STD_LOGIC;
19      lcd_dat         : inout  STD_LOGIC_VECTOR (3 downto 0);
20      lcd_rw          : out   STD_LOGIC;
21      lcd_rs          : out   STD_LOGIC;
22      lcd_e           : out   STD_LOGIC
23  );
24  end top;
25
26  architecture Behavioral of top is
27
28
29      signal intern_clk      : STD_LOGIC;
30      signal count_set_gain_sig : STD_LOGIC_VECTOR (8 downto 0);
31      signal Send_Button_Pressed : STD_LOGIC;
32      signal clk_50kHz      : STD_LOGIC;
33      signal count          : STD_LOGIC_VECTOR (12 downto 0);
34      signal z1             : STD_LOGIC_VECTOR (3 downto 0);
35      signal z2             : STD_LOGIC_VECTOR (3 downto 0);
36      signal z3             : STD_LOGIC_VECTOR (3 downto 0);
37      signal r1             : STD_LOGIC_VECTOR (3 downto 0);
38      signal r2             : STD_LOGIC_VECTOR (3 downto 0);
39      signal r3             : STD_LOGIC_VECTOR (3 downto 0);
40      signal SPI_read_HighNibble : STD_LOGIC_VECTOR (3 downto 0);
41      signal SPI_read_LowNibble  : STD_LOGIC_VECTOR (3 downto 0);
42
43
44
45
46
47      COMPONENT setgain is
48      PORT (
49          amp_cs      : out   STD_LOGIC;
50          clock       : in    STD_LOGIC;
51          sdi         : out   STD_LOGIC;
52          sck_out     : out   STD_LOGIC;
53          busy        : out   STD_LOGIC;
54          SPI_read_HighNibble : out   STD_LOGIC_VECTOR (3 downto 0);
55          SPI_read_LowNibble  : out   STD_LOGIC_VECTOR (3 downto 0);
56          amp_do      : in    STD_LOGIC;
57          count       : in    STD_LOGIC_VECTOR (8 downto 0)
58      );
59  end COMPONENT;
60
61

```



```
top.vhd                                     Wed Jun 18 16:23:08 2008
62
63 COMPONENT count_set_gain is
64   PORT (
65     clock       : in  STD_LOGIC;
66     start_button : in  STD_LOGIC;
67     button_pressed : in STD_LOGIC;
68     count_set_gain_i : inout STD_LOGIC_VECTOR( 8 downto 0)
69   );
70
71 end COMPONENT;
72
73
74 COMPONENT counter_lcd is
75   PORT (
76     clock : in  STD_LOGIC;
77     count : inout STD_LOGIC_VECTOR (12 downto 0)
78   );
79 end COMPONENT;
80
81
82 COMPONENT divider_lcd is
83   Port (
84     ext_clk_50MHz      : in  STD_LOGIC;
85     dev_clock_out      : inout STD_LOGIC
86   );
87 end COMPONENT;
88
89 COMPONENT mac_lcd is
90   PORT ( clock       : in  STD_LOGIC;
91     lcd_dat      : out  STD_LOGIC_VECTOR (3 downto 0);
92     lcd_e        : out  STD_LOGIC;
93     lcd_rw       : out  STD_LOGIC;
94     count        : in  STD_LOGIC_VECTOR (12 downto 0);
95     lcd_rs       : out  STD_LOGIC;
96     z1           : in  STD_LOGIC_VECTOR (3 downto 0);
97     z2           : in  STD_LOGIC_VECTOR (3 downto 0);
98     z3           : in  STD_LOGIC_VECTOR (3 downto 0);
99     r1           : in  STD_LOGIC_VECTOR (3 downto 0);
100    r2           : in  STD_LOGIC_VECTOR (3 downto 0);
101    r3           : in  STD_LOGIC_VECTOR (3 downto 0)
102  );
103 end COMPONENT;
104
105 COMPONENT set_gain_z_lcd is
106   PORT (
107     z1           : out  STD_LOGIC_VECTOR (3 downto 0);
108     z2           : out  STD_LOGIC_VECTOR (3 downto 0);
109     z3           : out  STD_LOGIC_VECTOR (3 downto 0);
110     r1           : out  STD_LOGIC_VECTOR (3 downto 0);
111     r2           : out  STD_LOGIC_VECTOR (3 downto 0);
112     r3           : out  STD_LOGIC_VECTOR (3 downto 0);
113     SPI_read_LowNibble : in  STD_LOGIC_VECTOR (3 downto 0);
114     SPI_read_HighNibble : in  STD_LOGIC_VECTOR (3 downto 0);
115     clk          : in  STD_LOGIC
116   );
117 end COMPONENT;
118
119
120
121
122
```



```
top.vhd                                     Wed Jun 18 16:23:08 2008
123     begin
124
125
126
127
128     Inst_set_gain_z_lcd: set_gain_z_lcd PORT MAP
129     (
130         z1             => z1,
131         z2             => z2,
132         z3             => z3,
133         r1             => r1,
134         r2             => r2,
135         r3             => r3,
136         SPI_read_HighNibble => SPI_read_HighNibble,
137         SPI_read_LowNibble  => SPI_read_LowNibble,
138         clk              => clk_system
139     );
140
141     Inst_counter_lcd: counter_lcd PORT MAP
142     (
143         clock => clk_50kHz,
144         count => count
145     );
146
147     Inst_mac_lcd: mac_lcd PORT MAP
148     (
149         clock      => clk_50kHz,
150         lcd_dat    => lcd_dat,
151         lcd_e      => lcd_e,
152         lcd_rw     => lcd_rw,
153         lcd_rs     => lcd_rs,
154         z1         => z1,
155         z2         => z2,
156         z3         => z3,
157         r1         => r1,
158         r2         => r2,
159         r3         => r3,
160         count      => count
161     );
162
163     Inst_divider_lcd: divider_lcd PORT MAP
164     (
165         ext_clk_50MHz => clk_system,
166         dev_clock_out => clk_50kHz
167     );
168
169
170
171     Inst_setgain: setgain PORT MAP
172     (
173         amp_cs      => amp_cs,
174         clock       => clk_system,
175         sdi         => sdi,
176         amp_do      => amp_do,
177         sck_out     => sck_out,
178         busy        => Send_Button_Pressed,
179         SPI_read_HighNibble => SPI_read_HighNibble,
180         SPI_read_LowNibble  => SPI_read_LowNibble,
181         count       => count_set_gain_sig
182     );
183
```



```
top.vhd                                     Wed Jun 18 16:23:08 2008
184
185
186
187
188     Inst_count_set_gain: count_set_gain PORT MAP
189     (
190         clock      => clk_system,
191         start_button => start_button,
192         count_set_gain_i => count_set_gain_sig,
193         button_pressed => Send_Button_Pressed
194     );
195
196     end Behavioral;
197
```



```

mac_lcd.vhd                                     Wed Jun 18 16:23:20 2008
1
2 -----
3 --Projekt: Verstärkung anzeigen
4 --Instanz: Mac_LCD
5 -----
6 library IEEE;
7 use IEEE.STD_LOGIC_1164.ALL;
8 use IEEE.STD_LOGIC_ARITH.ALL;
9 use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11 entity mac_lcd is
12 PORT ( clock      : in   STD_LOGIC;
13       lcd_dat     : out  STD_LOGIC_VECTOR (3 downto 0);
14       lcd_e       : out  STD_LOGIC;
15       lcd_rw      : out  STD_LOGIC;
16       count       : in   STD_LOGIC_VECTOR (12 downto 0);
17       lcd_rs      : out  STD_LOGIC;
18       z1          : in   STD_LOGIC_VECTOR (3 downto 0);
19       z2          : in   STD_LOGIC_VECTOR (3 downto 0);
20       z3          : in   STD_LOGIC_VECTOR (3 downto 0);
21       r1          : in   STD_LOGIC_VECTOR (3 downto 0);
22       r2          : in   STD_LOGIC_VECTOR (3 downto 0);
23       r3          : in   STD_LOGIC_VECTOR (3 downto 0);
24 );
25 end mac_lcd;
26
27 architecture Behavioral of mac_lcd is
28 begin
29
30
31 process (clock)
32 variable Init_LCD_finished: STD_LOGIC := '0';
33 begin
34 if rising_edge (clock) then
35 if Init_LCD_finished = '0' Then
36 case count is
37 when "0001011101110" => lcd_dat <= "0011"; ----750
38                        lcd_e  <= '0';
39                        lcd_rs  <= '0';
40                        lcd_rw  <= '0';
41 when "0001011101111" => lcd_e  <= '1'; ----751
42 when "0001110111101" => lcd_e  <= '1'; ----957
43 when "0001111000011" => lcd_e  <= '1'; ----963
44 when "0001111000110" => lcd_dat <= "0010"; ----966
45 when "0001111000111" => lcd_e  <= '1'; ----967
46 when "0001111001010" => lcd_dat <= "0001"; -----
47 when "0001111001011" => lcd_e  <= '1';
48 when "0001111001110" => lcd_dat <= "1100"; --- function set
49 when "0001111001111" => lcd_e  <= '1'; -----
50 when "0001111010001" => lcd_dat <= "0000";
51 when "0001111010010" => lcd_e  <= '1'; ----- entry mode
52 when "0001111010100" => lcd_dat <= "0110";
53 when "0001111010101" => lcd_e  <= '1'; -----
54 when "0001111010110" => lcd_dat <= "0000";
55 when "0001111010111" => lcd_e  <= '1'; ----- display control
56 when "0001111011001" => lcd_dat <= "1100";
57 when "0001111011010" => lcd_e  <= '1'; -----
58 when "0001111011100" => lcd_dat <= "0000";
59 when "0001111011101" => lcd_e  <= '1'; --- display clear
60 when "0001111011111" => lcd_dat <= "0001";
61 when "0001111000000" => lcd_e  <= '1'; -----

```



```

mac_lcd.vhd                                     Wed Jun 18 16:23:20 2008
62      when "0011000000000" => lcd_dat <= "0000";
63      when "0011000000010" => lcd_e <= '1';
64      when "0011000000100" => lcd_dat <= "1101";
65      when "0011000000101" => lcd_e <= '1'; -----
66      when "0011000001000" => lcd_dat <= "0100";
67              lcd_rs <= '1';
68      when "0011000001010" => lcd_e <= '1';
69      when "0011000001100" => lcd_dat <= "0111";
70      when "0011000010000" => lcd_e <= '1'; ----- G
71 -----
72      when "0011000011000" => lcd_dat <= "0110";
73      when "0011000011011" => lcd_e <= '1';
74      when "0011000011110" => lcd_dat <= "0001";
75      when "0011000100010" => lcd_e <= '1'; ----- a
76 -----
77      when "0011000101000" => lcd_dat <= "0110";
78      when "0011000101011" => lcd_e <= '1';
79      when "0011000101111" => lcd_dat <= "1001";
80      when "0011000110010" => lcd_e <= '1'; ----- i
81 -----
82      when "0011000110100" => lcd_dat <= "0110";
83      when "0011000111000" => lcd_e <= '1';
84      when "0011000111010" => lcd_dat <= "1110";
85      when "0011000111100" => lcd_e <= '1'; ----- n
86 -----
87      when "0011000111110" => lcd_dat <= "0100";
88      when "0011001000001" => lcd_e <= '1';
89      when "0011001000100" => lcd_dat <= "0001";
90      when "0011001000111" => lcd_e <= '1'; ----- A
91 -----
92      when "0011001001001" => lcd_dat <= "0011";
93      when "0011001001011" => lcd_e <= '1';
94      when "0011001001101" => lcd_dat <= "1010";
95      when "0011001001111" => lcd_e <= '1'; ----- :
96 -----
97      when "0011001010001" => lcd_dat <= "0010";
98      when "0011001010011" => lcd_e <= '1';
99      when "0011001010101" => lcd_dat <= "0000";
100     when "0011001010111" => lcd_e <= '1'; -----
101 -----
102     when "0011001011001" => lcd_dat <= "0011";
103     when "0011001011011" => lcd_e <= '1';
104     when "0011001011101" => lcd_dat <= z1;
105     when "0011001011111" => lcd_e <= '1'; ----- z1
106 -----
107     when "0011001100011" => lcd_dat <= "0011";
108     when "0011001100110" => lcd_e <= '1';
109     when "0011001101001" => lcd_dat <= z2;
110     when "0011001101011" => lcd_e <= '1'; ----- z2
111 -----
112     when "0011001110000" => lcd_dat <= "0011";
113     when "0011001110010" => lcd_e <= '1';
114     when "0011001110100" => lcd_dat <= z3;
115     when "0011001110111" => lcd_e <= '1'; ----- z3
116 -----
117     when "0011010000000" => lcd_dat <= "0010";
118     when "0011010000011" => lcd_e <= '1';
119     when "0011010000101" => lcd_dat <= "0000";
120     when "0011010000100" => lcd_e <= '1'; -----
121 -----
122     when "0011010001100" => lcd_dat <= "0100";

```



```

mac_lcd.vhd                                     Wed Jun 18 16:23:20 2008
123      when "0011010001110" => lcd_e  <= '1';
124      when "0011010010000" => lcd_dat <= "0010";
125      when "0011010010100" => lcd_e  <= '1';          ----- B
126
127      when "0011010011100" => lcd_dat <= "0011";
128      when "0011010011110" => lcd_e  <= '1';
129      when "0011010100000" => lcd_dat <= "1010";
130      when "0011010100100" => lcd_e  <= '1';          ----- :
131
132      when "0011010110000" => lcd_dat <= "0011";
133      when "0011010110010" => lcd_e  <= '1';
134      when "0011010110100" => lcd_dat <= r1;
135      when "0011010110111" => lcd_e  <= '1';          ----- r1
136
137      when "0011100000000" => lcd_dat <= "0011";
138      when "0011100000010" => lcd_e  <= '1';
139      when "0011100000100" => lcd_dat <= r2;
140      when "0011100000111" => lcd_e  <= '1';          ----- r2
141
142      when "0011100100000" => lcd_dat <= "0011";
143      when "0011100100010" => lcd_e  <= '1';
144      when "0011100100100" => lcd_dat <= r3;
145      when "0011100100111" => lcd_e  <= '1';          ----- r3
146
147
148      when "1111111111111" => Init_LCD_finished := '1';
149      when others          => lcd_e  <= '0';
150  end case;
151
152
153
154
155  elsif Init_LCD_finished = '1' then
156  case count is
157
158      when "0000000000000" => lcd_dat <= "0000";
159                          lcd_rs <= '0';
160      when "0000000000011" => lcd_e  <= '1';
161      when "0000000001110" => lcd_dat <= "0001";
162      when "0000000010010" => lcd_e  <= '1';          ----- CURSOR HOME
163
164      when "0011000000101" => lcd_rs <= '1';
165      when "0011000001000" => lcd_dat <= "0100";
166      when "0011000001010" => lcd_e  <= '1';
167      when "0011000001100" => lcd_dat <= "0111";
168      when "0011000010000" => lcd_e  <= '1';          ----- G
169
170      when "0011000011000" => lcd_dat <= "0110";
171      when "0011000011011" => lcd_e  <= '1';
172      when "0011000011110" => lcd_dat <= "0001";
173      when "0011000100010" => lcd_e  <= '1';          ----- a
174
175      when "0011000101000" => lcd_dat <= "0110";
176      when "0011000101011" => lcd_e  <= '1';
177      when "0011000101111" => lcd_dat <= "1001";
178      when "0011000110010" => lcd_e  <= '1';          ----- i
179
180      when "0011000110100" => lcd_dat <= "0110";
181      when "0011000111000" => lcd_e  <= '1';
182      when "0011000110101" => lcd_dat <= "1110";
183      when "0011000111100" => lcd_e  <= '1';          ----- n

```



```

mac_lcd.vhd                                     Wed Jun 18 16:23:20 2008
184 -----
185 when "0011000111110" => lcd_dat <= "0100";
186 when "0011001000001" => lcd_e <= '1';
187 when "0011001000100" => lcd_dat <= "0001";
188 when "0011001000111" => lcd_e <= '1'; ----- A
189 -----
190 when "0011001001001" => lcd_dat <= "0011";
191 when "0011001001011" => lcd_e <= '1';
192 when "0011001001101" => lcd_dat <= "1010";
193 when "0011001001111" => lcd_e <= '1'; ----- :
194 -----
195 when "0011001010001" => lcd_dat <= "0010";
196 when "0011001010011" => lcd_e <= '1';
197 when "0011001010101" => lcd_dat <= "0000";
198 when "0011001010111" => lcd_e <= '1'; -----
199 -----
200 when "0011001011001" => lcd_dat <= "0011";
201 when "0011001011011" => lcd_e <= '1';
202 when "0011001011101" => lcd_dat <= z1;
203 when "0011001011111" => lcd_e <= '1'; ----- z1
204 -----
205 when "0011001100011" => lcd_dat <= "0011";
206 when "0011001100110" => lcd_e <= '1';
207 when "0011001101001" => lcd_dat <= z2;
208 when "0011001101011" => lcd_e <= '1'; ----- z2
209 -----
210 when "0011001110000" => lcd_dat <= "0011";
211 when "0011001110010" => lcd_e <= '1';
212 when "0011001110100" => lcd_dat <= z3;
213 when "0011001110111" => lcd_e <= '1'; ----- z3
214 -----
215 when "0011010000000" => lcd_dat <= "0010";
216 when "0011010000011" => lcd_e <= '1';
217 when "0011010000101" => lcd_dat <= "0000";
218 when "0011010001000" => lcd_e <= '1'; -----
219 -----
220 when "0011010001100" => lcd_dat <= "0100";
221 when "0011010001110" => lcd_e <= '1';
222 when "0011010010000" => lcd_dat <= "0010";
223 when "0011010010100" => lcd_e <= '1'; ----- B
224 -----
225 when "0011010011100" => lcd_dat <= "0011";
226 when "0011010011110" => lcd_e <= '1';
227 when "0011010100000" => lcd_dat <= "1010";
228 when "0011010100100" => lcd_e <= '1'; ----- :
229 -----
230 when "0011010110000" => lcd_dat <= "0011";
231 when "0011010110010" => lcd_e <= '1';
232 when "0011010110100" => lcd_dat <= r1;
233 when "0011010110111" => lcd_e <= '1'; ----- r1
234 -----
235 when "0011100000000" => lcd_dat <= "0011";
236 when "0011100000010" => lcd_e <= '1';
237 when "0011100000100" => lcd_dat <= z2;
238 when "0011100000111" => lcd_e <= '1'; ----- r2
239 -----
240 when "0011100100000" => lcd_dat <= "0011";
241 when "0011100100010" => lcd_e <= '1';
242 when "0011100100100" => lcd_dat <= z3;
243 when "0011100100111" => lcd_e <= '1'; ----- z3
244 -----

```





```
mac_lcd.vhd                                     Wed Jun 18 16:23:20 2008
245         when "11111111111111" => Init_LCD_finished := '1';
246         when others           => lcd_e   <= '0';
247
248     end case;
249 end if;
250 end if;
251
252 end process;
253 end Behavioral;
```



```

setgain.vhd                                     Wed Jun 18 16:23:30 2008
1
2  -----
3  --Projekt: Verstärkung anzeigen
4  --Instanz: Setgain
5  -----
6  library IEEE;
7  use IEEE.STD_LOGIC_1164.ALL;
8  use IEEE.STD_LOGIC_ARITH.ALL;
9  use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11  entity setgain is
12  PORT (
13      amp_cs          : out STD_LOGIC;
14      clock           : in  STD_LOGIC;
15      sdi             : out STD_LOGIC;
16      sck_out         : out STD_LOGIC;
17      amp_do          : in  STD_LOGIC;
18      busy            : out STD_LOGIC;
19      SPI_read_LowNibble : out STD_LOGIC_VECTOR (3 downto 0);
20      SPI_read_HighNibble : out STD_LOGIC_VECTOR (3 downto 0);
21      count           : in  STD_LOGIC_VECTOR (8 downto 0)
22  );
23  end setgain;
24
25  architecture Behavioral of setgain is
26
27      signal gain : STD_LOGIC_VECTOR (7 downto 0) := "00010101" ;
28
29      -----
30      --gain -1 : 0001
31      --      -2 : 0010
32      --      -5 : 0011
33      --      -10 : 0100
34      --      -20 : 0101
35      --      -50 : 0110
36      --      -100: 0111
37      -----
38  begin
39
40
41  process (clock)
42  begin
43      if rising_edge (clock) THEN
44
45          case count is
46              when "000000000" => amp_cs <= '1';
47                                  sdi   <= '0';
48                                  busy  <= '0';
49                                  sck_out <= '0';
50
51              when "000000001" => busy <= '1';
52              when "000001100" => sdi   <= '0';    --10
53                                  amp_cs <= '0';
54
55              when "000010100" => sdi   <= gain(7);--20
56              when "000011001" => sck_out <= '1';    --25
57                                  SPI_read_HighNibble(3)<= amp_do;
58
59              when "000110010" => sck_out <= '0';    --50
60
61              when "000111111" => sdi   <= gain(6);--63
62
63              when "001001011" => sck_out <= '1';    --75
64                                  SPI_read_HighNibble(2)<= amp_do;
65
66              when "001100100" => sck_out <= '0';    --100
67
68              when "001110001" => sdi   <= gain(5);--113

```



```
setgain.vhd                                     Wed Jun 18 16:23:30 2008
62         when "001111101" => sck_out <= '1'; --125
63             SPI_read_HighNibble(1)<= amp_do;
64         when "010010110" => sck_out <= '0'; --150
65         when "010101101" => sdi    <= gain(4);--163
66         when "010101111" => sck_out <= '1'; --175
67             SPI_read_HighNibble(0)<= amp_do;
68         when "011001000" => sck_out <= '0'; --200
69         when "011010101" => sdi    <= gain(3);--213
70         when "011100001" => sck_out <= '1'; --225
71             SPI_read_LowNibble(3)<= amp_do;
72         when "011111010" => sck_out <= '0'; --250
73         when "100000111" => sdi    <= gain(2);--263
74         when "100010011" => sck_out <= '1'; --275
75             SPI_read_LowNibble(2)<= amp_do;
76         when "100101100" => sck_out <= '0'; --300
77         when "100111001" => sdi    <= gain(1);--313
78         when "101000011" => sck_out <= '1'; --325
79             SPI_read_LowNibble(1)<= amp_do;
80         when "101011110" => sck_out <= '0'; --350
81         when "101101011" => sdi    <= gain(0);--363
82         when "101110111" => sck_out <= '1'; --375
83             SPI_read_LowNibble(0)<= amp_do;
84         when "110010000" => sck_out <= '0'; --400
85         when "110010111" => sdi    <= '0'; --413
86         when "111000010" => amp_cs  <= '1'; --450
87         when "111000011" => busy   <= '0'; --451
88         when others      =>
89             end case;
90         end if;
91     end process;
92 end Behavioral;
```



```
count_set_gain.vhd                                     Wed Jun 18 16:23:37 2008
1  -----
2  --Projekt: Verstärkung anzeigen
3  --Instanz: Count_Set_Gain
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12
13  entity count_set_gain is
14
15      PORT (
16          clock           : in  STD_LOGIC;
17          start_button    : in  STD_LOGIC;
18          button_pressed  : in  STD_LOGIC;
19          count_set_gain_i : inout STD_LOGIC_VECTOR ( 8 downto 0) := "000000000";
20      );
21
22  end count_set_gain;
23
24  architecture Behavioral of count_set_gain is
25
26  begin
27
28  process (clock)
29  begin
30
31      if rising_edge (clock) THEN
32
33          if start_button = '0' AND count_set_gain_i = "000000000" AND button_pressed = '0' THEN
34              count_set_gain_i <= "000000000";
35          end if;
36          if start_button = '1' AND count_set_gain_i = "000000000" THEN
37              count_set_gain_i <= "000000001";
38          end if;
39          if count_set_gain_i < "111000010" AND button_pressed = '1' THEN
40              count_set_gain_i <= count_set_gain_i + 1;
41          end if;
42          if count_set_gain_i = "111000010" AND start_button = '0' then
43              count_set_gain_i <= "111000011";
44          end if;
45          if count_set_gain_i = "111000011" AND button_pressed = '0' AND start_button = '0' THEN
46              count_set_gain_i <= count_set_gain_i + 1;
47          end if;
48          if count_set_gain_i > "111000011" THEN
49              count_set_gain_i <= "000000000";
50          end if;
51          end if;
52
53      end process;
54
55  end Behavioral;
56
57
```



```

set_gain_z_lcd.vhd                                     Wed Jun 18 16:23:45 2008
1  -----
2  --Projekt: Verstärkung anzeigen
3  --Instanz: Set_Gain_Z_LCD
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11
12  entity set_gain_z_lcd is
13  port (
14      z1          : out STD_LOGIC_VECTOR (3 downto 0);
15      z2          : out STD_LOGIC_VECTOR (3 downto 0);
16      z3          : out STD_LOGIC_VECTOR (3 downto 0);
17      r1          : out STD_LOGIC_VECTOR (3 downto 0);
18      r2          : out STD_LOGIC_VECTOR (3 downto 0);
19      r3          : out STD_LOGIC_VECTOR (3 downto 0);
20      SPI_read_LowNibble : in  STD_LOGIC_VECTOR (3 downto 0);
21      SPI_read_HighNibble : in  STD_LOGIC_VECTOR (3 downto 0);
22      clk         : in  STD_LOGIC
23  );
24  end set_gain_z_lcd;
25
26  architecture Behavioral of set_gain_z_lcd is
27
28  begin
29  Process (clk)
30  begin
31      if rising_edge (clk) THEN
32          case SPI_read_LowNibble is
33              WHEN "0001" => z1 <= "0000";
34                          z2 <= "0000";          -- GainA: 001
35                          z3 <= "0001";
36              WHEN "0010" => z1 <= "0000";
37                          z2 <= "0000";          -- GainA: 002
38                          z3 <= "0010";
39              WHEN "0011" => z1 <= "0000";
40                          z2 <= "0000";          -- GainA: 005
41                          z3 <= "0101";
42              WHEN "0100" => z1 <= "0000";
43                          z2 <= "0001";          -- GainA: 010
44                          z3 <= "0000";
45              WHEN "0101" => z1 <= "0000";
46                          z2 <= "0010";          -- GainA: 020
47                          z3 <= "0000";
48              WHEN "0110" => z1 <= "0000";
49                          z2 <= "0101";          -- GainA: 050
50                          z3 <= "0000";
51              WHEN "0111" => z1 <= "0001";
52                          z2 <= "0000";          -- GainA: 100
53                          z3 <= "0000";
54              WHEN OTHERS => z1 <= "1111";
55                          z2 <= "1111";          -- Gain: ???
56                          z3 <= "1111";
57          end case;
58
59          case SPI_read_HighNibble is
60              WHEN "0001" => r1 <= "0000";
61                          r2 <= "0000";          -- GainB: 001

```



```
set_gain_z_lcd.vhd                                     Wed Jun 18 16:23:45 2008
62                                                     r3 <= "0001";
63     WHEN "0010" => r1 <= "0000";
64     r2 <= "0000"; -- GainB: 002
65     r3 <= "0010";
66     WHEN "0011" => r1 <= "0000";
67     r2 <= "0000"; -- GainB: 005
68     r3 <= "0101";
69     WHEN "0100" => r1 <= "0000";
70     r2 <= "0001"; -- GainB: 010
71     r3 <= "0000";
72     WHEN "0101" => r1 <= "0000";
73     r2 <= "0010"; -- GainB: 020
74     r3 <= "0000";
75     WHEN "0110" => r1 <= "0000";
76     r2 <= "0101"; -- GainB: 050
77     r3 <= "0000";
78     WHEN "0111" => r1 <= "0001";
79     r2 <= "0000"; -- GainB: 100
80     r3 <= "0000";
81     WHEN OTHERS => r1 <= "1111";
82     r2 <= "1111"; -- GainB: ???
83     r3 <= "1111";
84     end case;
85     end if ;
86     end process;
87     end Behavioral;
88
89
```



```
counter_lcd.vhd                                     Wed Jun 18 16:23:52 2008
1  -----
2  --Projekt: Verstärkung anzeigen
3  --Instanz: Counter_LCD
4  -----
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.STD_LOGIC_ARITH.ALL;
8  use IEEE.STD_LOGIC_UNSIGNED.ALL;
9
10
11  entity counter_lcd is
12  port (
13      clock : in STD_LOGIC;
14      count : inout STD_LOGIC_VECTOR (12 downto 0)
15  );
16  end counter_lcd;
17
18  architecture Behavioral of counter_lcd is
19
20  begin
21  process (clock)
22  begin
23      if rising_edge (clock) THEN
24          count <= count + '1';
25      end if;
26  end process;
27  end Behavioral;
28
29
```



```
divider_lcd.vhd                                     Wed Jun 18 16:23:59 2008
1
2 -----
3 --Projekt: Verstärkung anzeigen
4 --Instanz: Divider_LCD
5 -----
6 library IEEE;
7 use IEEE.STD_LOGIC_1164.ALL;
8 use IEEE.STD_LOGIC_ARITH.ALL;
9 use IEEE.STD_LOGIC_UNSIGNED.ALL;
10
11
12
13 entity divider_lcd is
14     Port (
15         ext_clk_50MHz      : in    STD_LOGIC;
16         dev_clock_out     : inout  STD_LOGIC
17     );
18 end divider_lcd;
19
20
21 architecture Behavioral of divider_lcd is
22     signal divide_counter : integer := 0;
23
24
25 begin
26
27     Process(ext_clk_50MHz)
28     begin
29         if (rising_edge (ext_clk_50MHz)) then
30             if (divide_counter /= 1000) then
31                 divide_counter <= divide_counter + 1;
32             else
33                 divide_counter <= 0;
34                 dev_clock_out <= not (dev_clock_out);
35             end if;
36         end if;
37     end process;
38 end Behavioral;
39
40
41
```





```
top.ucf                                     Wed Jun 18 16:24:07 2008
1      #-----
2      #Projekt: Verstärkung anzeigen
3      #   User Constraint File
4      #-----
5      INST "Inst_setgain/amp_cs" INIT = 1;
6      INST "Inst_setgain/sck_out" INIT = 0;
7      NET "amp_cs"      LOC = "n7"  ;
8      NET "amp_do"      LOC = "e18" ;
9      NET "clk_system"  LOC = "c9"  ;
10     NET "lcd_dat<0>"   LOC = "r15" ;
11     NET "lcd_dat<1>"   LOC = "r16" ;
12     NET "lcd_dat<2>"   LOC = "p17" ;
13     NET "lcd_dat<3>"   LOC = "m15" ;
14     NET "lcd_e"        LOC = "m18" ;
15     NET "lcd_rs"       LOC = "l18" ;
16     NET "lcd_rw"       LOC = "l17" ;
17     NET "sck_out"      LOC = "u16" ;
18     NET "sdi"          LOC = "t4"  ;
19     NET "start_button" LOC = "K17" | PULLDOWN ;
20
```



## Literatur

- [Rei01] Jürgen Reichard, Bernd Schwarz . *VHDL-Synthese: Entwurf digitaler Schaltungen; 2Aufl.* Oldenbourg Wissenschaftsverlag GmbH, München, 2001.
- [Tiet03] Ulrich Tietze, Christoph Schenk. *Halbleiter-Schaltungstechnik; 12Aufl.* Springer-Verlag, Berlin, 2003.
- [Urb03] Klaus Urbanski, Roland Weitowitz. *Digitaltechnik; 4Aufl.* Springer-Verlag, Berlin, 2003.
- [Wann98] Markus Wannemacher. *Das FPGA-Kochbuch; 1Aufl.* International Thomson Publishing GmbH, Bonn, 1998.